

Parallel Opposite Diodes in Series with a Resistor: DC Input Measured vs. Input Potentials

