

Parallel Opposite Diodes in Series with a Resistor: Sinusoidal Input Measured vs. Input Potentials

