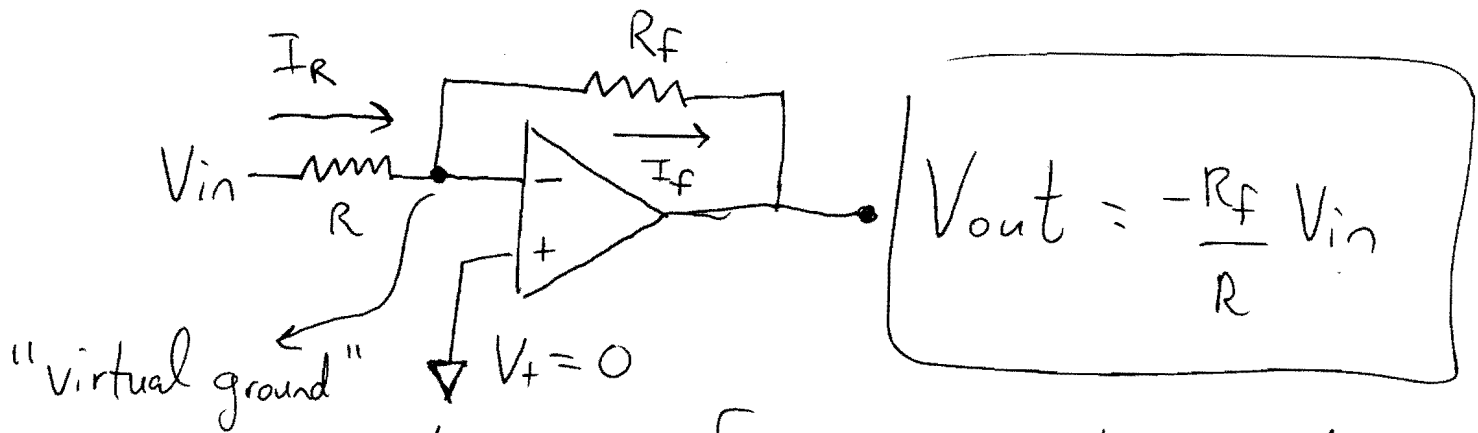


# Inverting Op-Amp :



Conservation of current yields

$$I_R = I_f, \text{ or}$$

$$\frac{V_{in} - V_-}{R} = \frac{V_- - V_{out}}{R_f}$$

Note that  $V_+ = \text{ground}$  and that

$G$  is very large thus  
So  $V_{out} \neq \pm V_{cc}$ .

$V_- = V_+ = 0$   
"virtual ground"


$$\frac{V_{in}}{R} = -\frac{V_{out}}{R_f} \quad (\text{when } V_- = 0)$$

$$\Rightarrow V_{out} = -\frac{R_f}{R} V_{in}$$

(1)
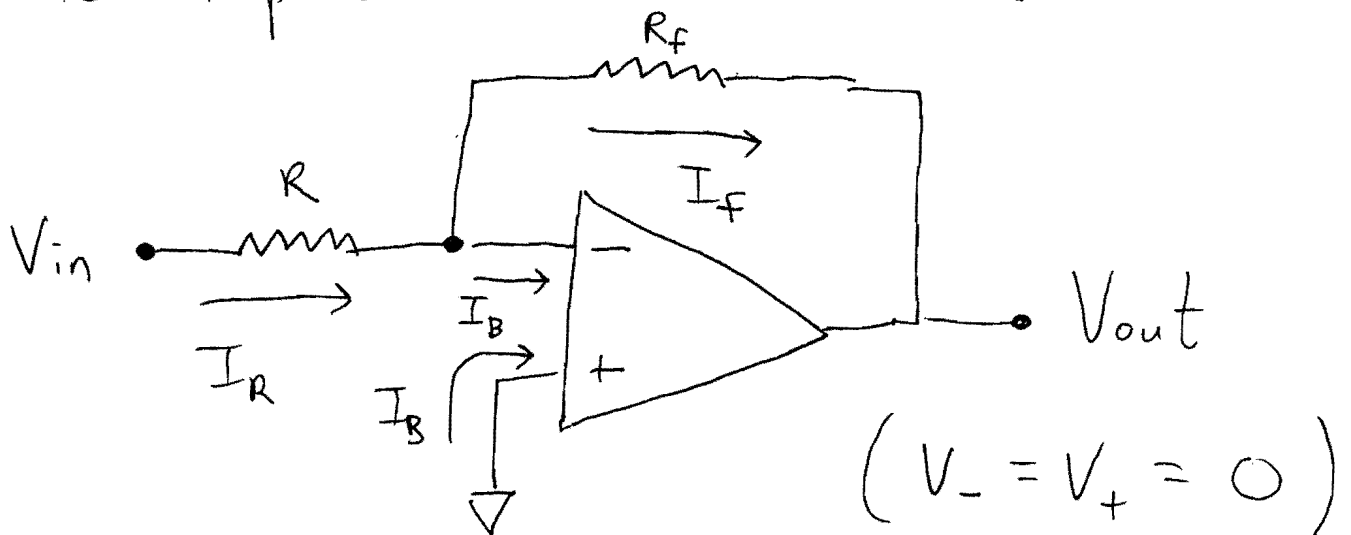
## Input Bias Current :

On the last page  $I_R = I_f$ , but this is not true in reality due to input bias current.



Use  $I_R = I_B + I_f$


or  $\frac{V_{in}}{R} = I_B - \frac{V_{out}}{R_f}$

"bias current correction"

$$V_{out} = -\frac{R_f}{R} V_{in} + I_B R_f$$

(2)

Correcting  $I_B$  error :

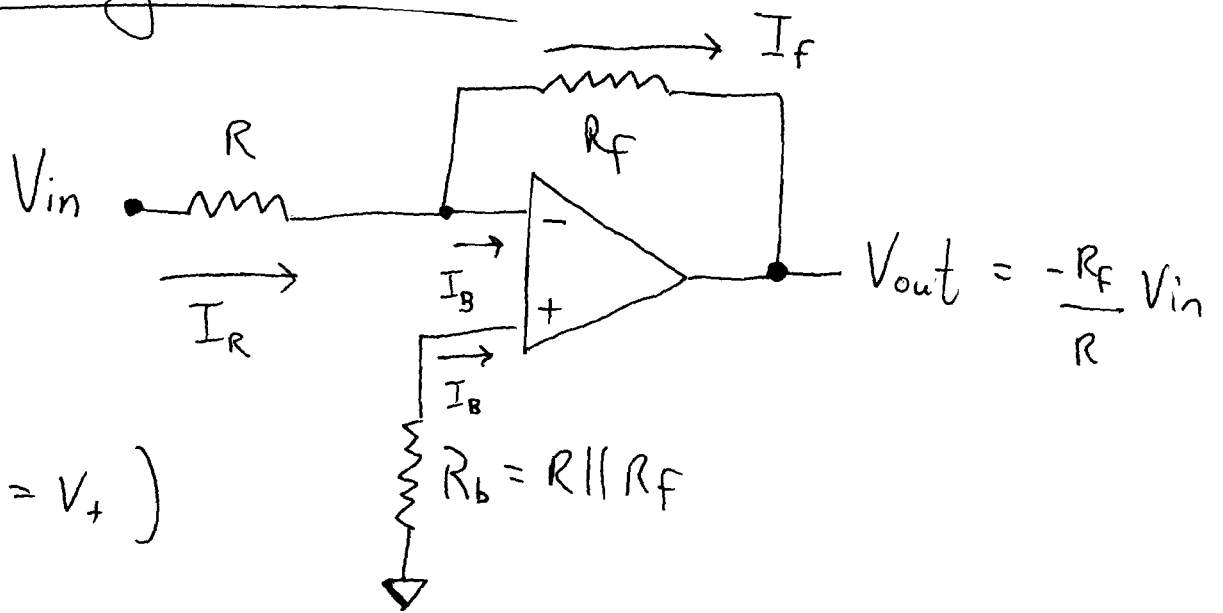

Conservation of current yields,

$$I_R = I_B + I_f$$

$$\rightarrow \frac{V_{in} - V_-}{R} = I_B + \frac{V_- - V_{out}}{R_f}$$

Use  $V_- = V_+$  yields ;

$$\frac{V_{in}}{R} - V_+ \left( \frac{1}{R} + \frac{1}{R_f} \right) - I_B = \frac{-V_{out}}{R_f}$$

(3)

$$\frac{V_{in}}{R} - V_+ \left( \frac{1}{R} + \frac{1}{R_f} \right) - I_B = -\frac{V_{out}}{R_f}$$

$\underbrace{\hspace{10em}}_{(R \parallel R_f)^{-1}}$

$$\frac{V_{in}}{R} - V_+ (R \parallel R_f)^{-1} - I_B = -\frac{V_{out}}{R_f}$$

From the circuit  $(0 - V_+) = I_B R \parallel R_f$

So,  $I_B = V_+ \left( \frac{1}{R} + \frac{1}{R_f} \right)$


$$V_{out} = -\frac{R_f}{R} V_{in}$$


4

# Inverting Amp Potential formalism

You can also solve for  $V_{out}$  using potentials instead of conservation of current. It's important with all of these examples to remember that  $G = G(\omega)$  is not constant. Sometimes you need to use that.

## General Divider :

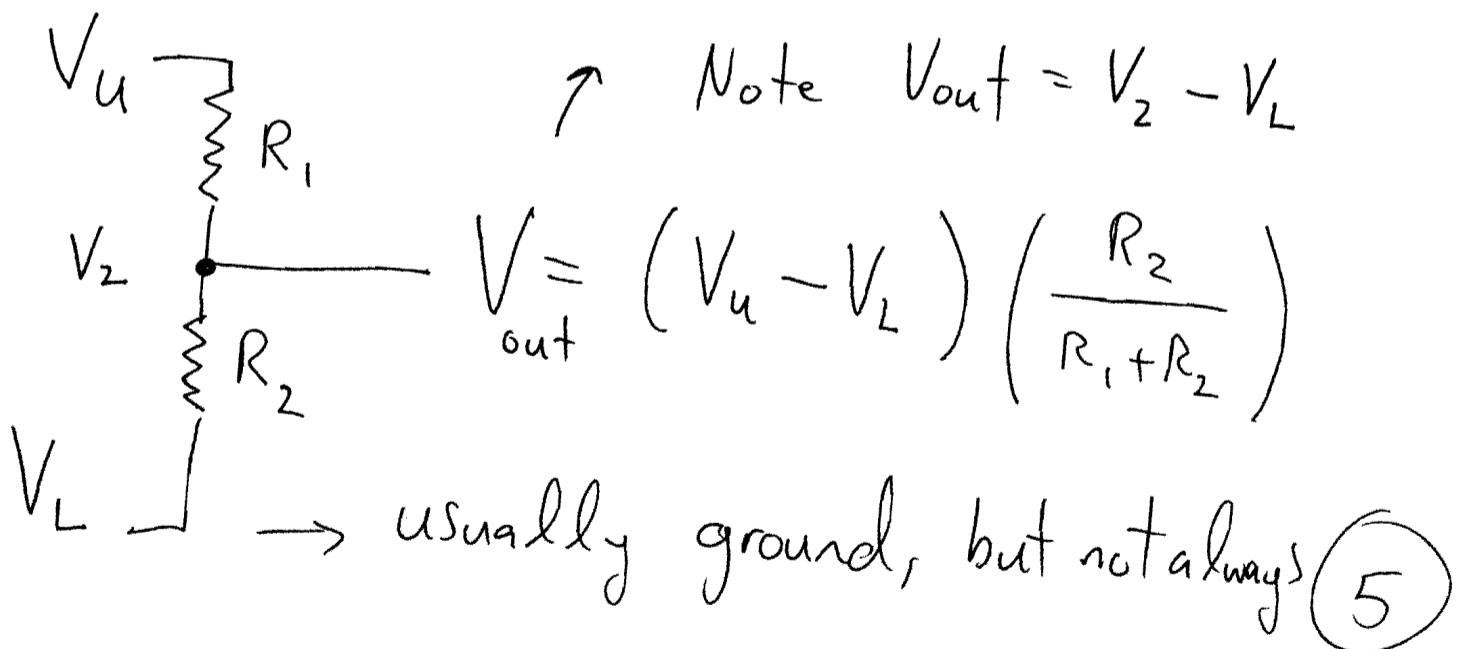

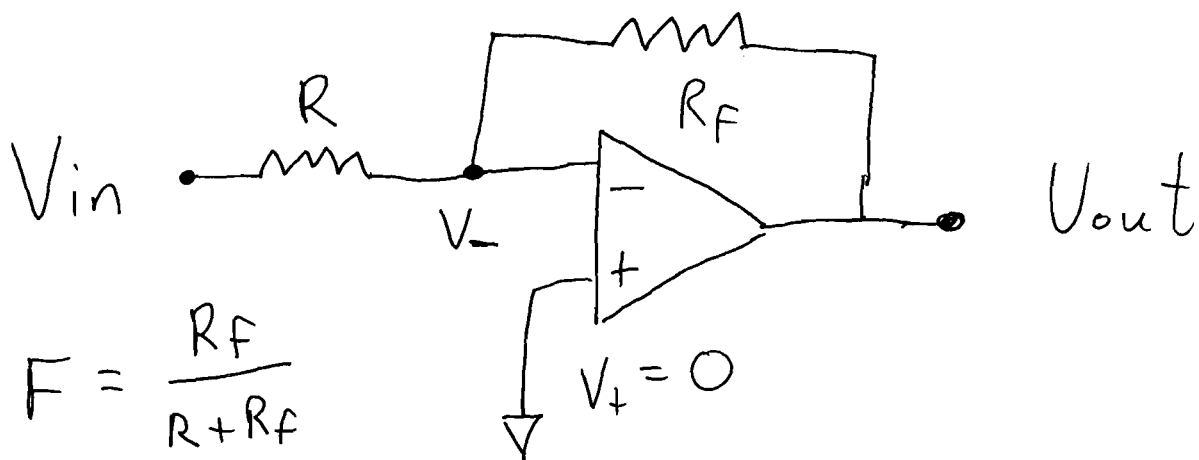

$$F = \frac{R_F}{R + R_F}$$

Use the general divider scheme to calculate  $V_{out}$ .

$$V_- - V_{out} = F (V_{in} - V_{out})$$

$$V_- = F V_{in} + V_{out} (1 - F)$$

$$\overline{V_{out} = G (V_+ - V_-)}$$

$$V_{out} = G (0 - F V_{in} - V_{out} (1 - F))$$

$$V_{out} = -G F V_{in} - G (1 - F) V_{out}$$

$$V_{out} (1 + G (1 - F)) = -G F V_{in}$$

6

$$V_{out} (G(1-F)) \approx -GF V_{in}$$

$$V_{out} \approx \left( \frac{-F}{1-F} \right) V_{in}$$

$$\frac{-F}{1-F} = -\frac{R_f}{R}$$

$$V_{out} \approx -\frac{R_f}{R} V_{in}$$

If  $\omega$  is large, then you cannot make the  $G$  large approximation, and you have to use the total equation. (7)