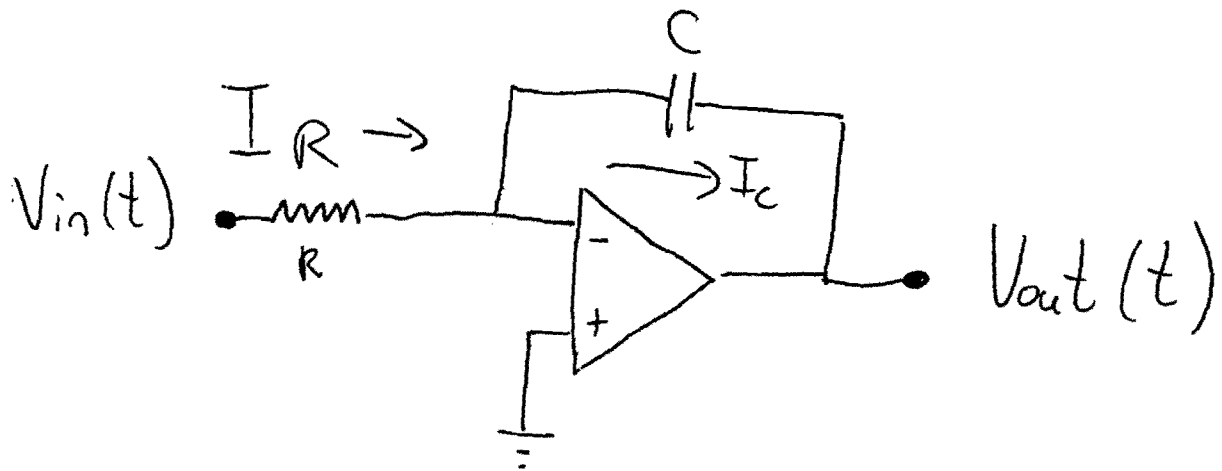


Op-Amp Filters :

(1)

Integrating (Low Pass) Filter :



As with most inverting configurations use conservation of current.


$$I_R = \frac{V_{in} - V_-}{R} ; \quad I_C = \frac{dQ_C}{dt} = C \frac{dV_C}{dt}$$

Use $V_- = 0$ $\rightarrow I_C = C \frac{d}{dt} (V_- - V_{out})$

$$\frac{V_{in}(t)}{R} = -C \frac{d}{dt} V_{out}(t)$$

$$\Rightarrow V_{out}(t) = -\frac{1}{RC} \int_0^t V_{in}(t') dt'$$

2

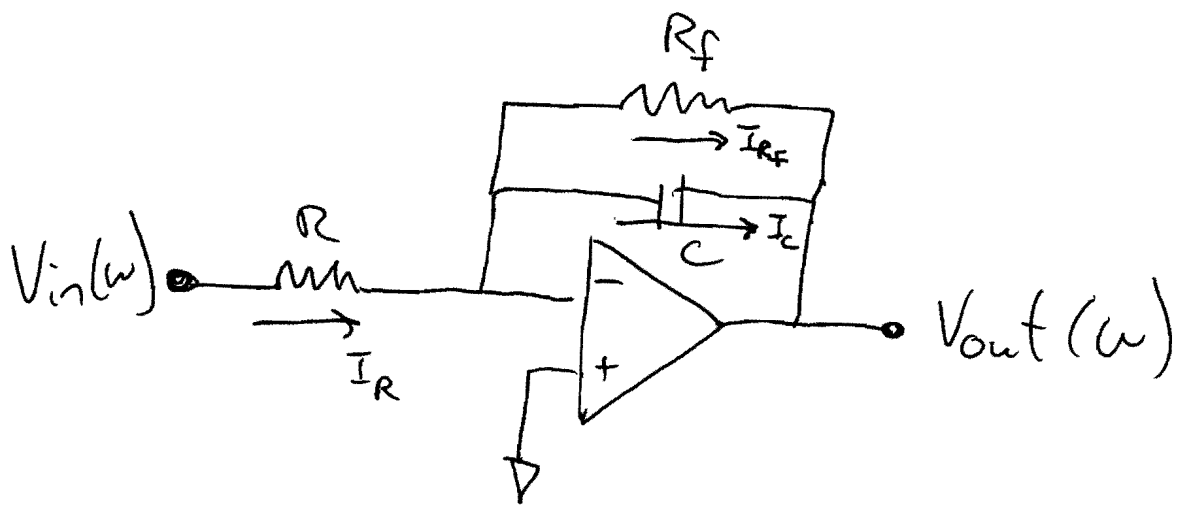

$$\bar{I}_R = \frac{V_{in}}{R} \quad ; \quad \bar{I}_C = \frac{V_C}{Z_C} = -i\omega C V_{out}(\omega)$$


$$\bar{I}_{RF} = -\frac{V_{out}}{R_f} \quad ; \quad \bar{I}_R = \bar{I}_C + \bar{I}_{RF}$$

↪
$$\frac{V_{in}}{R} = -V_{out} \left(i\omega C + \frac{1}{R_f} \right)$$

$$V_{out}(\omega) = -\frac{R_f}{R} \cdot \left(\frac{1}{i\omega C R_f + 1} \right) V_{in}(\omega)$$

Differentiating (High Pass Filter) Filter:

(3)

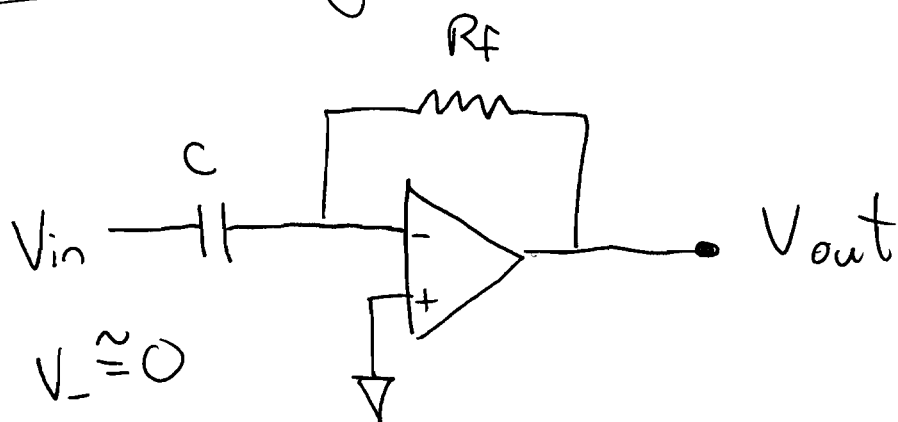

time domain : $V_{in} = V_{in}(t)$, $V_{out} = V_{out}(t)$

$$I_C = C \frac{dV_{in}}{dt} ; I_{Rf} = \frac{-V_{out}}{Rf} ; I_C = I_{Rf}$$

$$\Rightarrow V_{out}(t) = -R_f C \frac{dV_{in}(t)}{dt}$$

frequency domain


$$V_{in} = V_{in}(\omega)$$
$$V_{out} = V_{out}(\omega)$$

$$I_C = \frac{V_C}{Z_C} = -i\omega C V_{in}(\omega) ; I_{Rf} = \frac{-V_{out}(\omega)}{Rf}$$

$$\Rightarrow V_{out}(\omega) = -i\omega R_f C V_{in}(\omega)$$

Band Pass Filter :

(4)

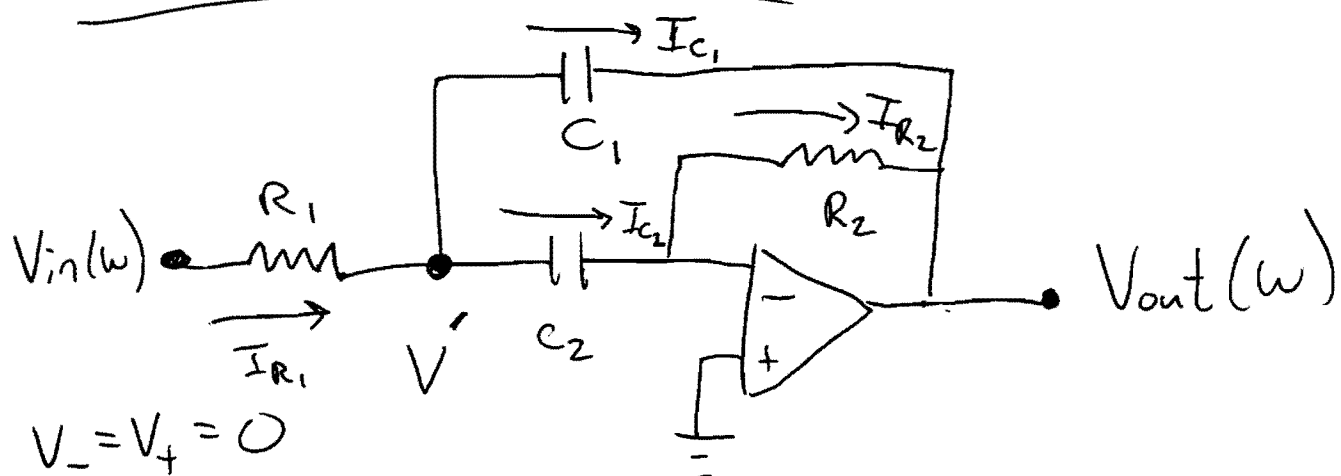

$$\bar{I}_{R_1} = \frac{V_{in} - V'}{R_1} ; \quad \bar{I}_{C_2} = -i\omega C_2 V'$$

$$\bar{I}_{R_2} = \frac{-V_{out}}{R_2} ; \quad \bar{I}_{C_1} = -(V' - V_{out}) i\omega C_1$$

① $\bar{I}_{R_1} = \bar{I}_{C_1} + \bar{I}_{C_2}$

② $\bar{I}_{C_2} = \bar{I}_{R_2}$

Use two equations to remove V' variable and solve for V_{out} .

$$V_{out}(\omega) = \frac{(-i\omega C_2 R_2) V_{in}(\omega)}{i\omega R_1 (C_1 + C_2) + C_1 C_2 R_1 R_2 \omega^2 - 1}$$