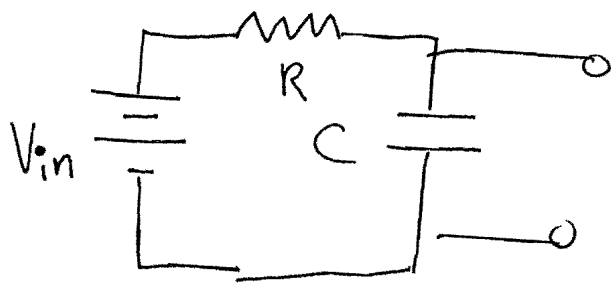


RC Filters :

(1)



$$V_{out} = \left(\frac{z_c}{z_c + R} \right) V_{in}$$

z_c = impedance of the capacitor = $\frac{1}{i\omega C}$

Recall that $\omega = 2\pi f$.

Also, the transmission function is defined by $A(\omega) = \frac{V_{out}}{V_{in}}$,


which is just the divider ratio.

$$A(\omega) = \frac{z_c}{z_c + R} = \frac{1/i\omega C}{1/i\omega C + R}$$

$A(\omega)$ is complex and we want to find its magnitude and phase.

Complex Plane :

(2)

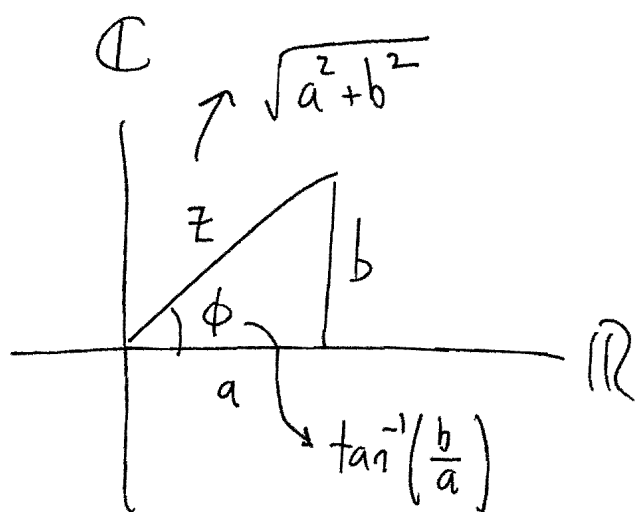

$$z = a + ib$$


$$|z|^2 = a^2 + b^2$$

$$\tan(\phi) = \frac{b}{a}, \phi = \tan^{-1}\left(\frac{b}{a}\right)$$

I want to mention that both $z_1 = a + ib$ and $z_2 = a - ib$ have the same magnitude ($\sqrt{a^2 + b^2}$) because the magnitude of a complex number is defined

by $|z|^2 = z^* z$, where

z^* is the complex conjugate of z .

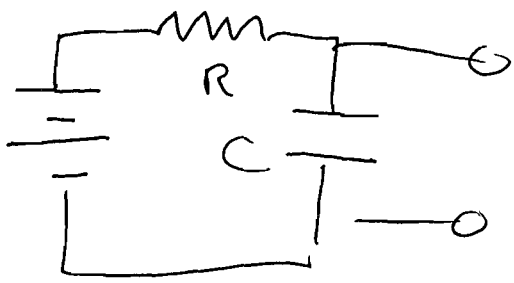

$$A(\omega) = \frac{1/i\omega C}{1/i\omega C + R}$$

③

The elegant way to solve all these transmission functions is to put them in $\frac{1}{a \pm ib}$ form, then use complex analysis on the denominator.

$$A(\omega) = \frac{1/i\omega C}{1/i\omega C + R} = \frac{1}{1 + i\omega RC}$$

Now the denominator looks

like $a + ib$ where $a = 1$

and $b = \omega RC$.

$$A(\omega) = \frac{1}{1+i\omega RC} = \frac{1}{\sqrt{1+(\omega RC)^2}} e^{i\phi} \quad (4)$$

$$\phi = ? \rightarrow \phi = \tan^{-1}\left(\frac{\omega RC}{1}\right), \text{ therefore}$$

$$A(\omega) = \frac{1}{\sqrt{1+(\omega RC)^2}} e^{i \tan^{-1}(\omega RC)}$$

or

$$A(\omega) = \frac{e^{-i \tan^{-1}(\omega RC)}}{\sqrt{1+(\omega RC)^2}}$$