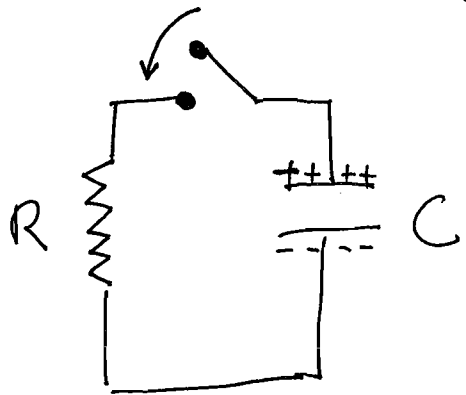


RC Time-Domain Analysis :

①

In general time domain analysis employs Kirchoff's energy conservation rule to create a differential equation which we need to solve.

RC Discharge Time :




Consider a capacitor that is charged with Q . When you close the switch and complete

the circuit how does the charge on the capacitor behave as a function of time?

o

Solution:

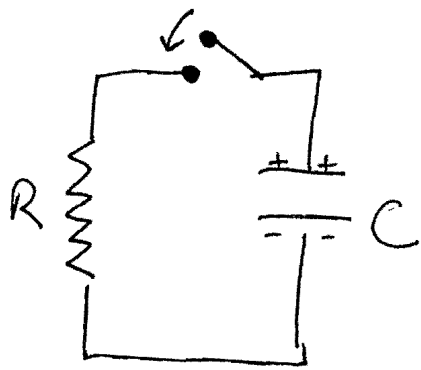

After closing the switch, (2)
At some instant in time the voltage across the resistor equals the voltage across the capacitor. (Measurement polarity is important)

① $V_R = V_C$ where $V_R = IR$, $V_C = \frac{Q}{C}$

So ① becomes $\frac{Q}{C} = IR$

② Now $I = -\frac{dQ}{dt}$ (losing charge)

$\Rightarrow \frac{Q}{C} = -R \frac{dQ}{dt}$ or $\boxed{\frac{dQ}{dt} = -\frac{1}{RC} Q}$


$\Rightarrow \boxed{Q(t) = e^{-t/RC}}$

Recall $I(t) = \frac{dQ(t)}{dt}$

and $V_C(t) = \frac{Q(t)}{C}$

RC Charging Time :

3

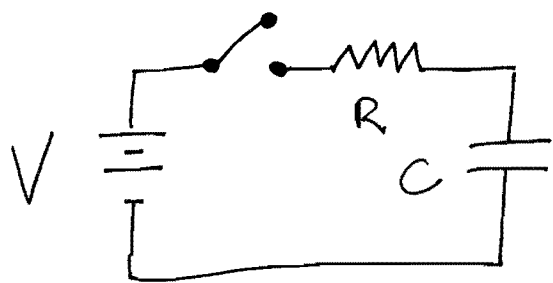

Now charge the "empty" capacitor with a battery.
What is $Q(t)$?

$$\textcircled{1} \sum_{\text{closed loop}} \underline{\Phi} = 0 = V - IR - \frac{Q}{C}$$

$$\textcircled{2} \text{Substitute } I = \frac{dQ}{dt} ; V - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

Rearrange...

$$\frac{dQ}{dt} = \frac{CV - Q}{RC} \Rightarrow \int_0^Q \frac{dQ'}{Q' - CV} = \int_0^t \frac{-dt}{RC}$$

$$\ln(Q' - CV) \Big|_{Q'=0}^{Q'=Q} = \frac{-t}{RC}$$

$$\frac{Q - CV}{-CV} = e^{-t/RC} \quad \text{or}$$

$$Q(t) = CV(1 - e^{-t/RC})$$