
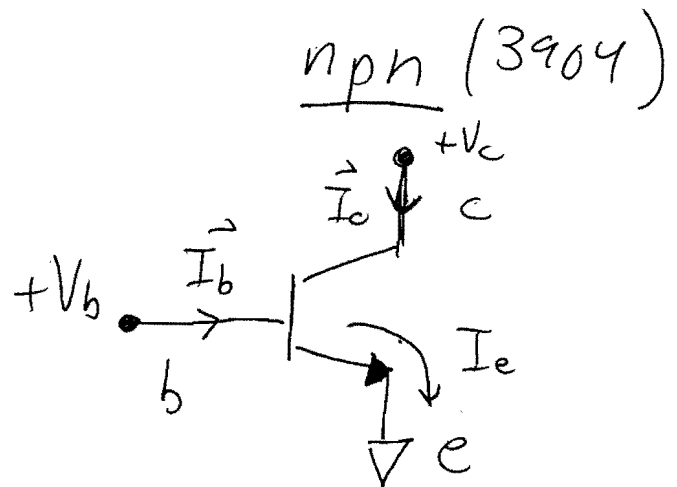

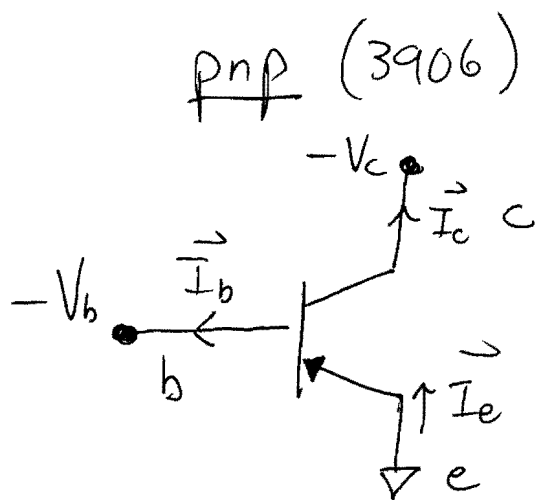
# Bipolar Junction Transistors :

Bipolar junction transistors (BJT's) are npn or pnp devices.




Notice how the emitter current flows forward bias for the b-e pn junction, and reverse bias for the c-b p-n junction.


Make sure you understand the "on" diagrams above before moving on.

①

# BJT response:

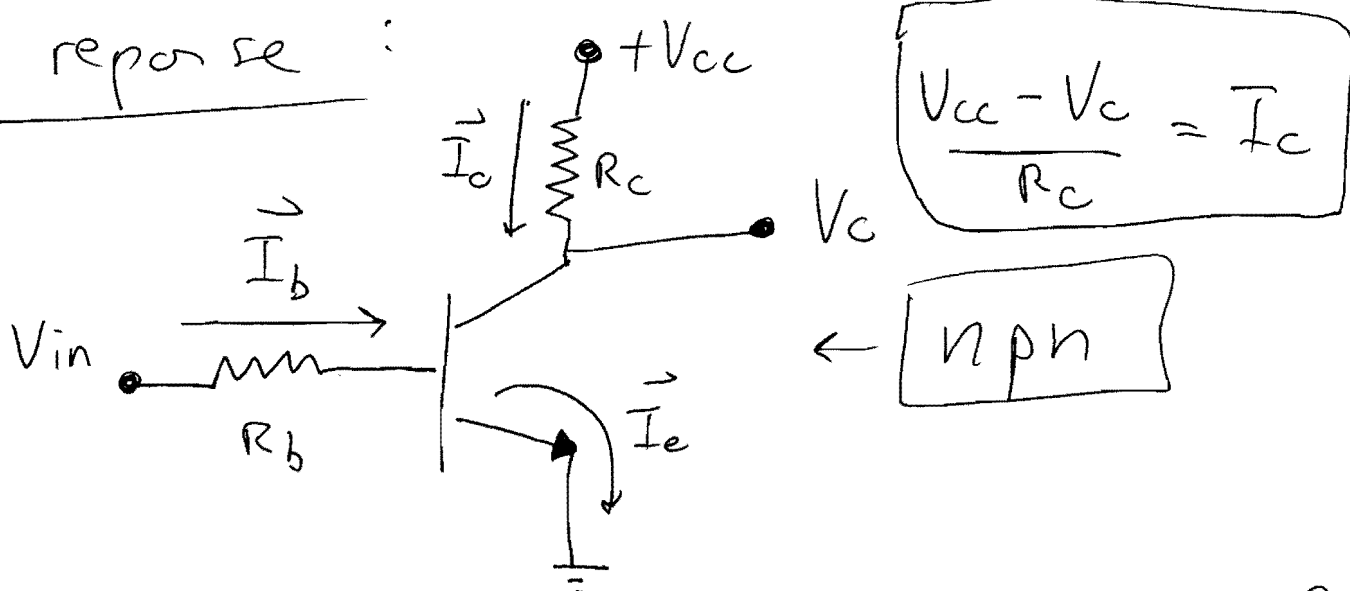


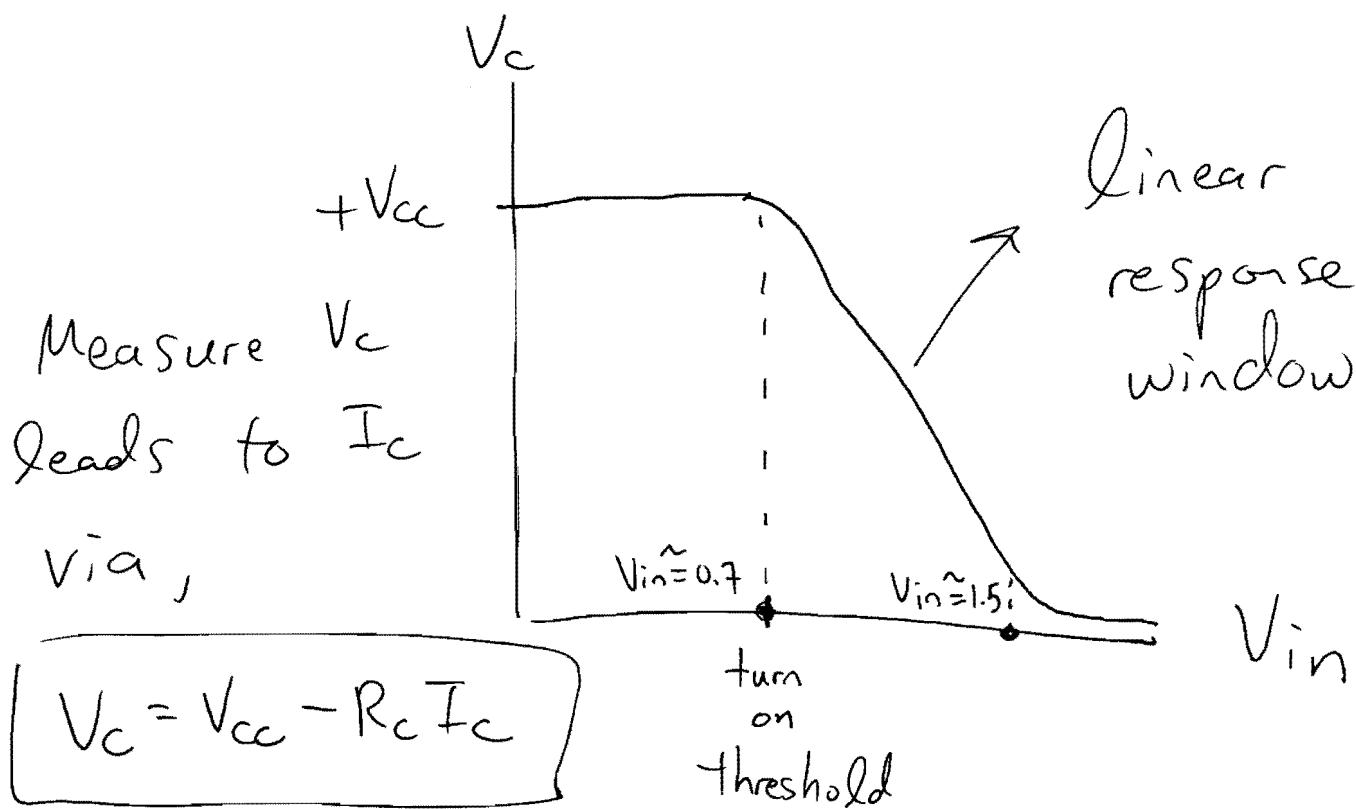Start off by applying a potential  $V_{in}$  to the base. Until you reach some threshold turn-on voltage  $V_c = V_{cc}$  because the transistor is off and there is no potential drop on  $R_c$ .


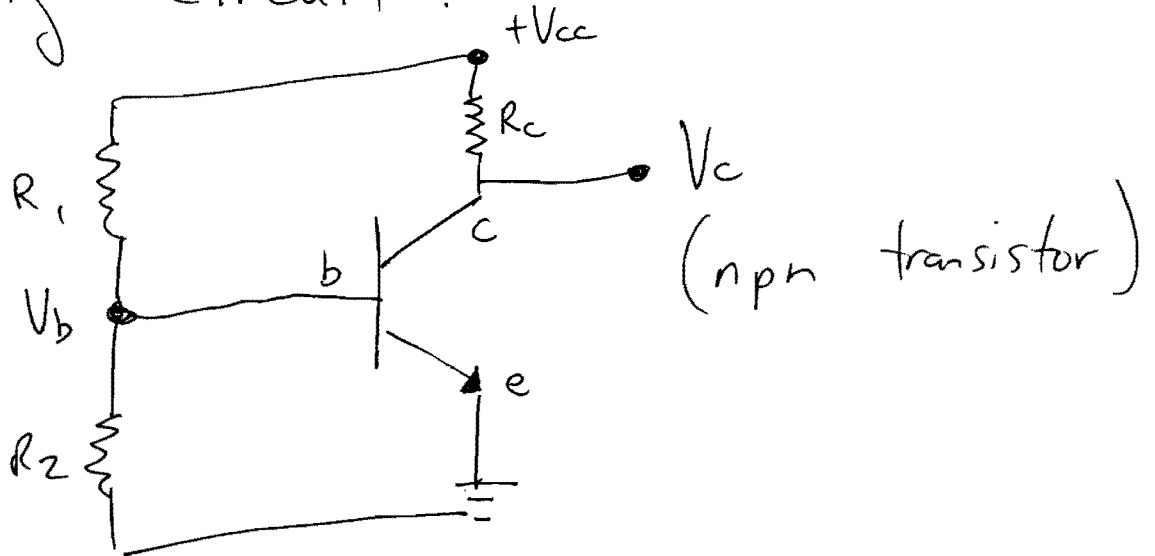
## Common Emitter Amplifier:


First you want to establish a DC Bias condition by making the following circuit.



The goal is to make  $V_c = \frac{V_{cc}}{2}$  so that you're operating right in the middle of the linear response window. Note that  $V_b = F V_{cc}$

where  $F = \frac{R_2}{R_1 + R_2}$ .

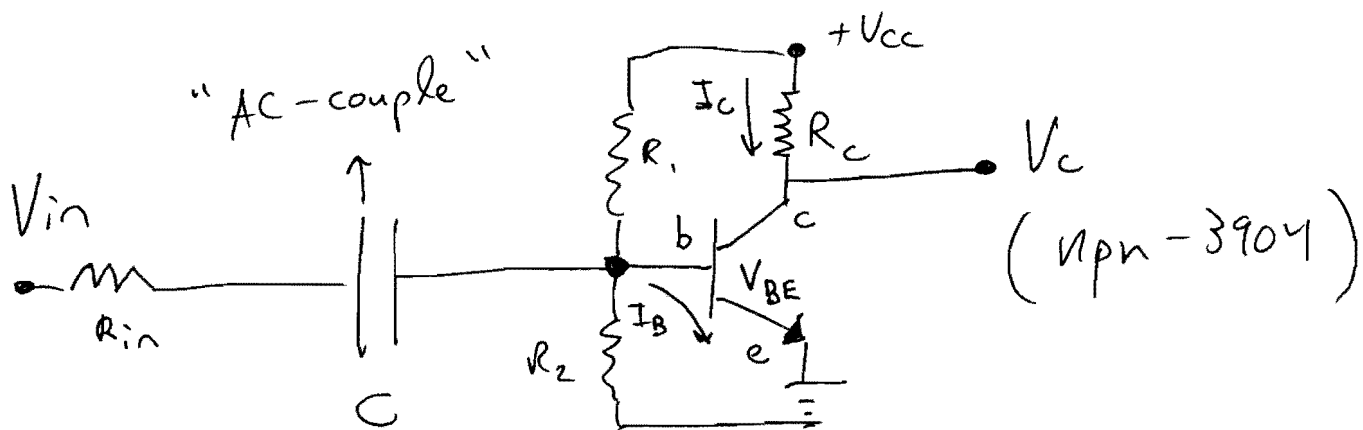Now that the proper DC-Bias condition is set up AC couple a signal (Capacitor) into the Common Emitter Amp.



①  $V_{cc} - V_c = I_c R_c$

②  $\beta = \frac{I_c}{I_B}$

③ so therefore  $V_{cc} - V_c = \beta I_B R_c$

What is  $V_{BE}$ ?

$$V_c = -\beta I_B R_c \quad (\text{AC coupled})$$


$$V_c = \underbrace{V_{cc}}_{\text{"DC term"}} - \beta I_B R_c \quad (\text{DC coupled})$$

④

Q: What is  $Z_{BE}$ ?

Soln:

Zoom in on the common emitter amplifier.

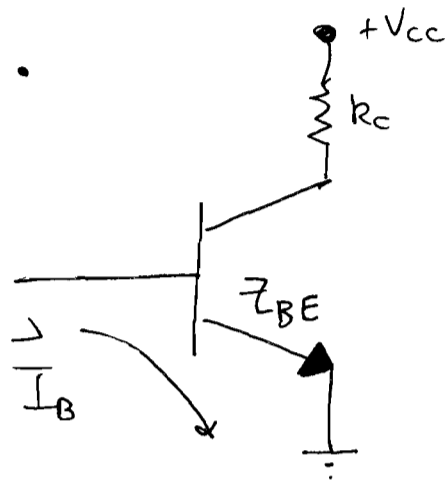

$Z_{BE}$  is a diode impedance.


$$I_D = I_0 (e^{\alpha V_D} - 1) \quad \text{So,} \quad \frac{1}{Z_D} = \frac{\partial I_D}{\partial V_D}$$

$$y_D = \frac{1}{Z_D} \approx \frac{1}{\alpha I_0 e^{\alpha V_D}} \approx \frac{1}{\alpha I_D}$$

$\frac{1}{Z_D} \approx \frac{1}{\alpha I_D}$  → measure  $I_B$   
gives you  $Z_{BE}$ !

(5)


# Measuring Base Current :

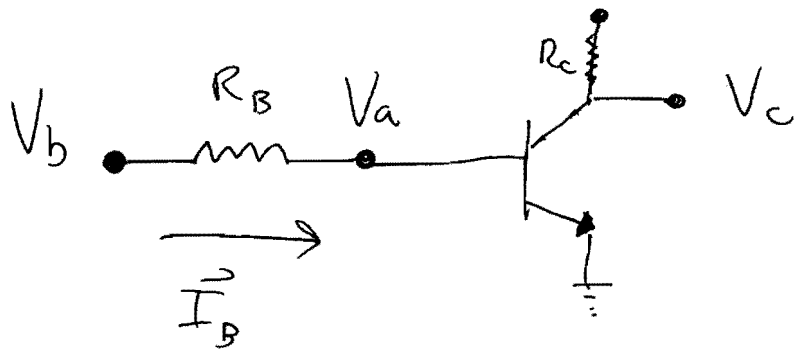

$$I_B = \frac{(V_b - V_a)}{R_B}, \text{ but we don't know } V_a.$$

Answer = Use Difference Amplifier.

# Difference Amplifier :

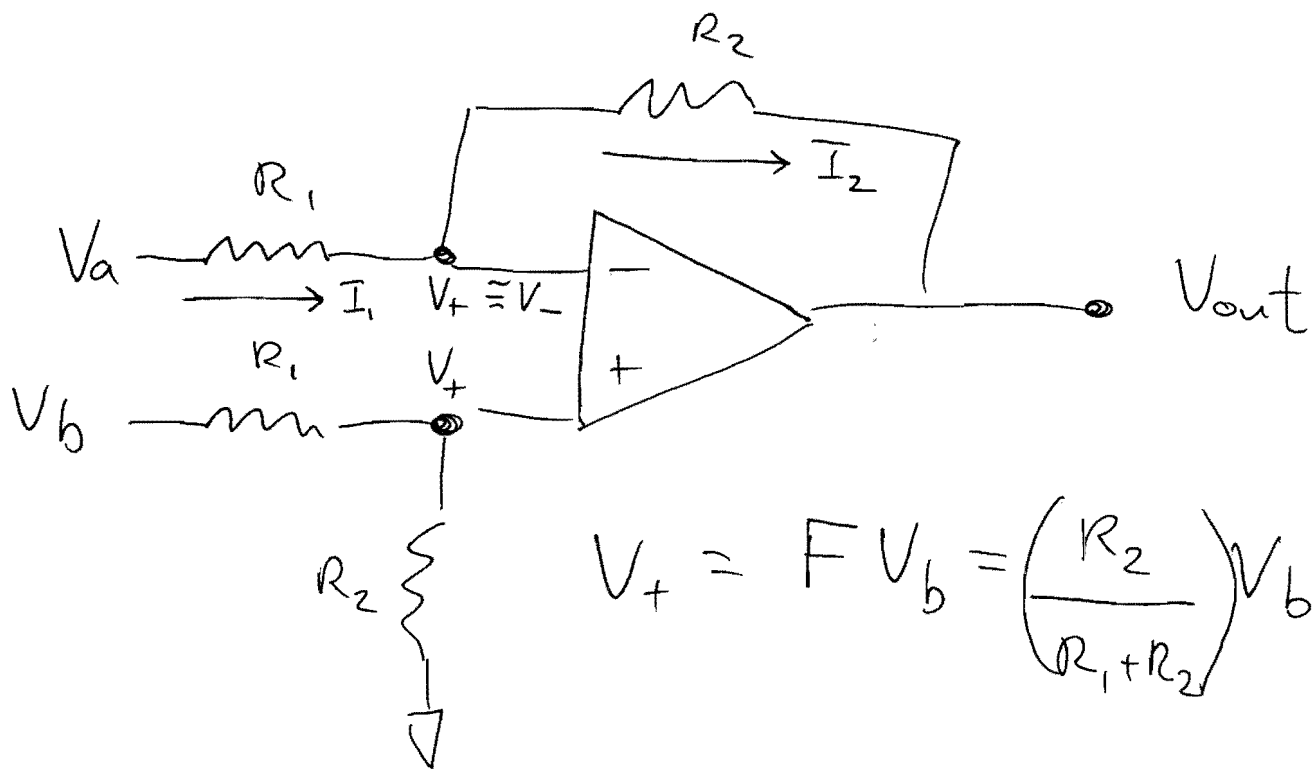

$$V_+ = F V_b = \left( \frac{R_2}{R_1 + R_2} \right) V_b$$

(6)


$$\underline{I_1 = I_2} \Rightarrow \frac{V_a - V_+}{R_1} = \frac{V_+ - V_{out}}{R_2}$$

and  $V_+ = FV_b$ , therefore

$$\frac{V_a - FV_b}{R_1} = \frac{FV_b - V_{out}}{R_2}$$



$$V_{out} = -\frac{R_2}{R_1} V_a + F\left(1 + \frac{R_2}{R_1}\right) V_b$$
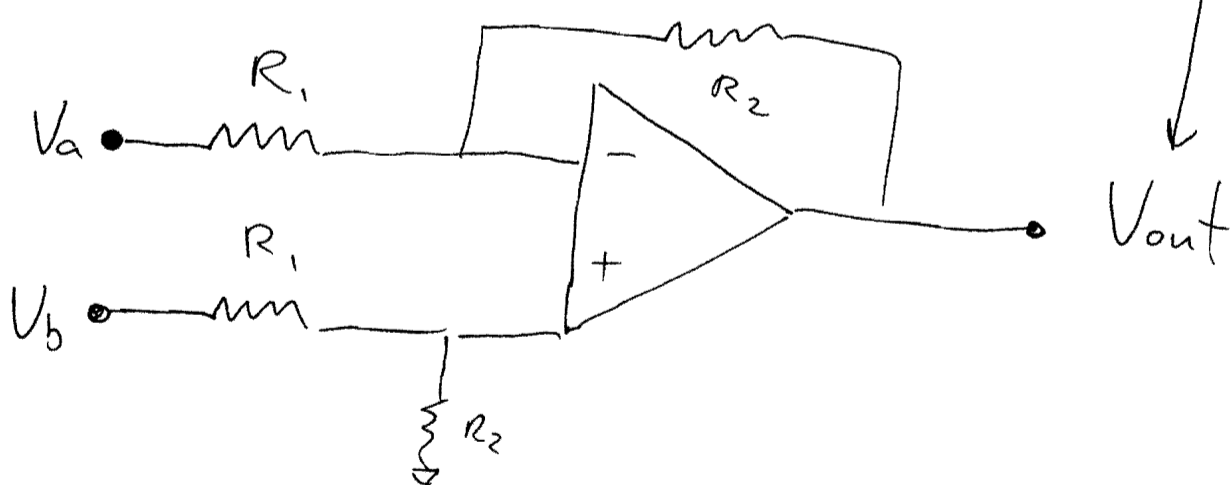
$$V_{out} = \frac{R_2}{R_1} (V_b - V_a)$$



(7)

# $\beta$ measurements :

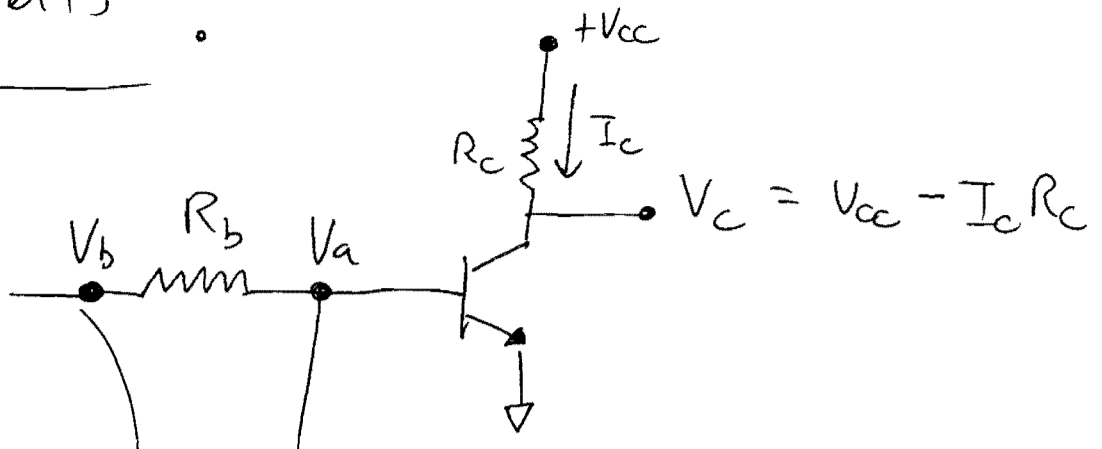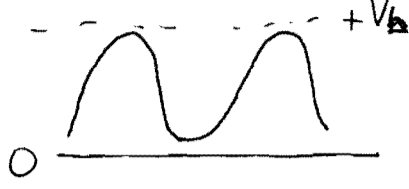



Diff. Amp.  $V = g(V_b - V_a)$

$$I_B = \frac{V_b - V_a}{R_b} = \frac{V}{gR_b}$$

$$V_c = V_{cc} - I_c R_c,$$

and  $\beta = \frac{I_c}{I_B}$ , so,

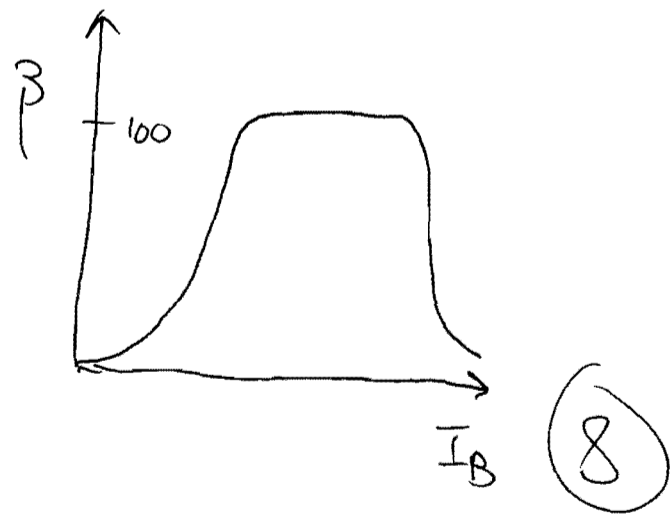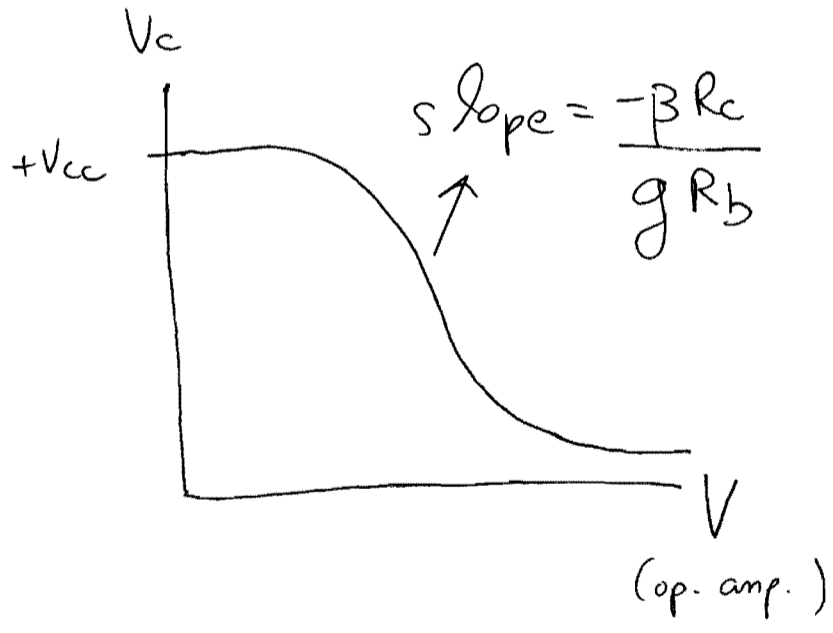
$$V_c = V_{cc} - \beta I_B R_c = V_{cc} - \frac{\beta V R_c}{gR_b} = V_c$$



8



# Common Collector Amplifier :

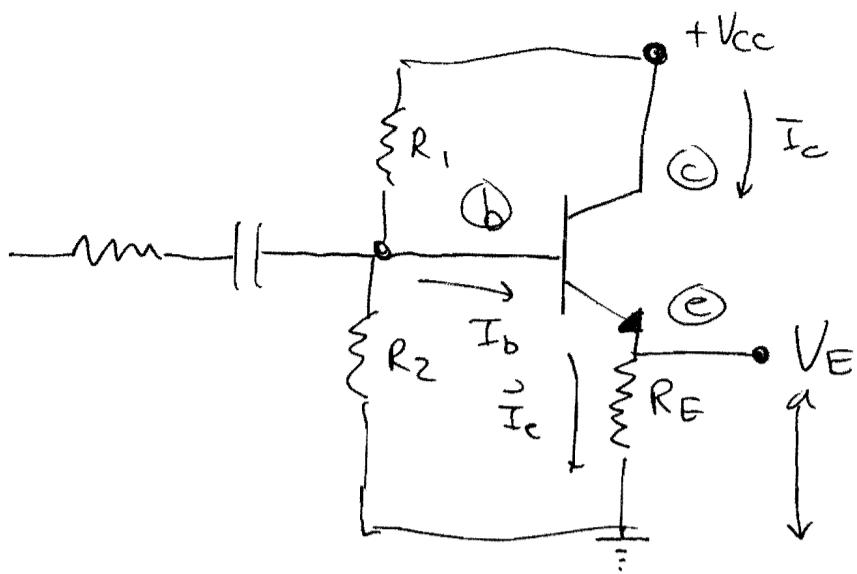

$$I_B \approx I_0 e^{\alpha (V_B - V_E)}$$

$$I_C = I_C + I_B \approx I_C$$

$$V_E = I_C R_E$$

E-potential = ?

$$V_E = I_C R_E = \beta I_B R_E = \beta R_E \underbrace{I_0 e^{\alpha (V_B - V_E)}}_{= I_B}$$

$$\ln V_E = \ln (\beta R_E I_0) + \alpha (V_B - V_E)$$

↓

$$\boxed{V_E = V_B \pm S}$$

$$\boxed{V_E = V_B - \frac{\ln V_E}{\alpha} + \frac{\ln \beta R_E I_0}{\alpha}} \quad (a)$$