

Ph 412 Lecture :


(2/13/2012)

The main topic is bipolar junction transistors, but starts w/ diode review.

Diodes: "pn-junction"

p-type = mobile holes \rightarrow Replace Si w/ group III.

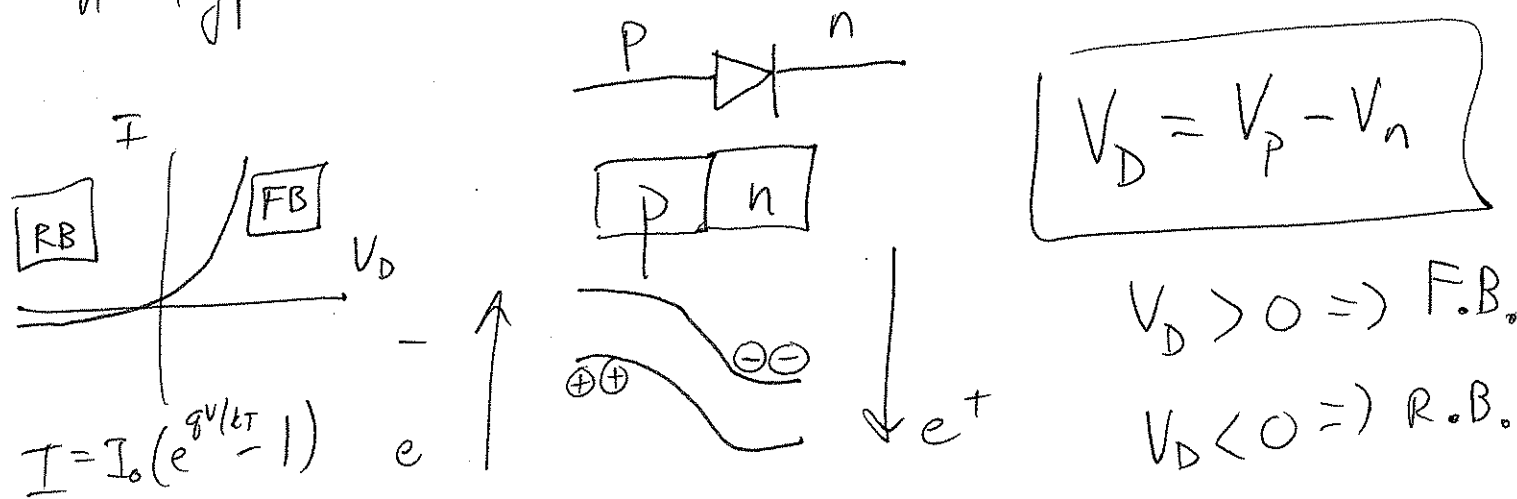n-type = mobile electrons \rightarrow Replace Si w/ group IV.




Adding $(+V)$ to the p-type region lowers the bands making it easier for current to flow.

Photodiodes: Send light into the depletion region to create $(+)(-)$ pairs.


LED
 $(+)(-)$ recombination

Photovoltaics

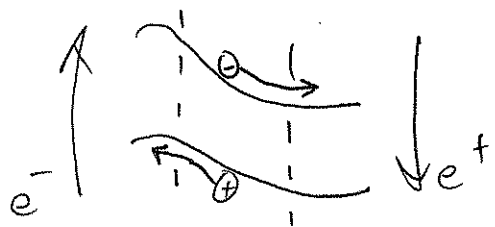
Resulting potential builds up from $(+)(-)$ separation. (1)



Band Diagrams / Gaps :

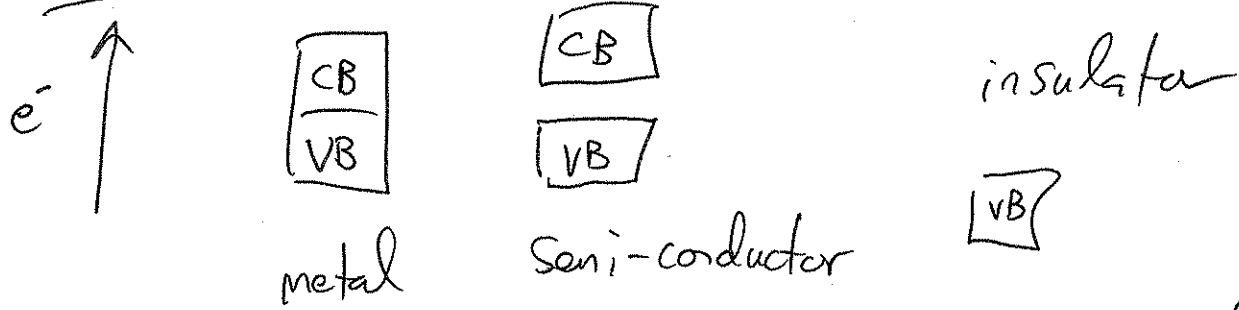

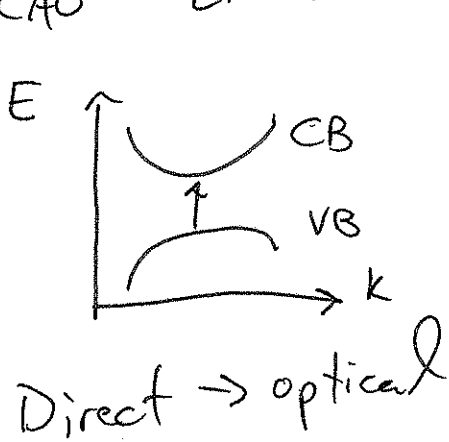
LCAO = Linear combination of atomic orbitals.



$$E = \hbar\omega$$

$$p = \hbar k$$

$$p = \frac{h}{\lambda} = \text{small}$$

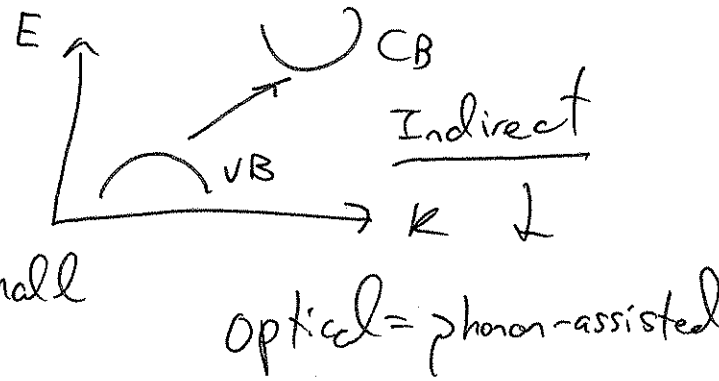

DFT ... briefly : (ψ_i) electrons

$$H\psi = E\psi \Rightarrow \left(\frac{-\hbar^2}{2m} \nabla^2 + V_{\text{eff}} \right) \psi_i = E_i \psi_i$$

$$\rho(r) = \sum_i^N |\psi_i(r)|^2$$

"Kohn-Sham Equations"
(1965)


$$V_{\text{eff}} = V_{\text{eff}}(\rho(r))$$

- iterate to find lowest E_i


BJT'S : Bipolar Junction Transistor

"pnp" or "npn"

pnp
3906

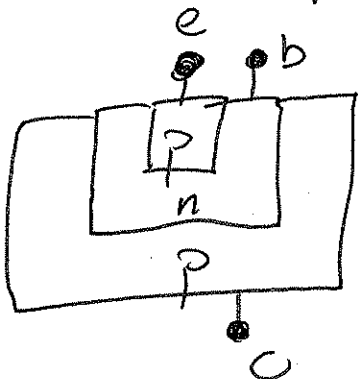


npn
3904

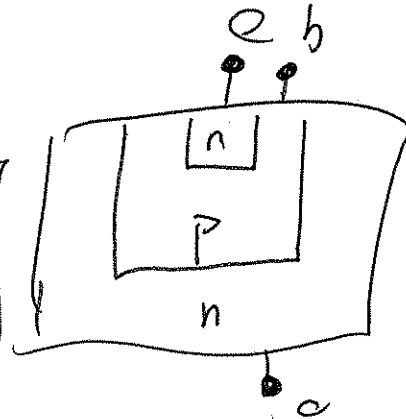


e = emitter
b = base
c = collector

pnp

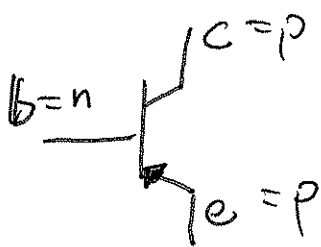


npn

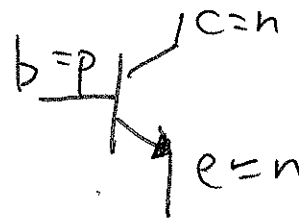

"On" Conditions


Forward bias b-e junction then repel collector current...

pnp

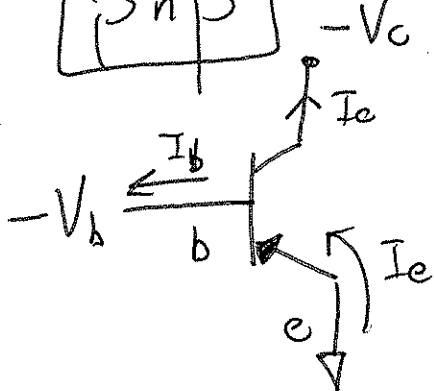

Use -V for pnp


npn

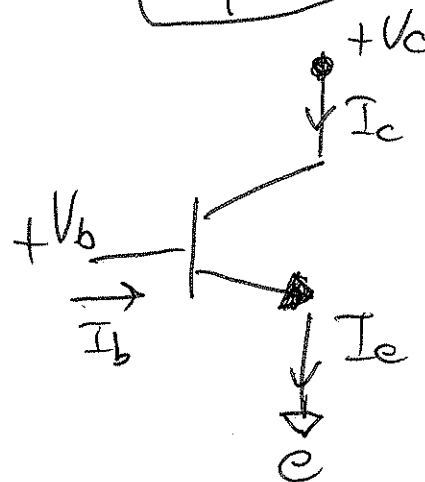

Use +V for npn

Current Gain :

Using pnp BJT

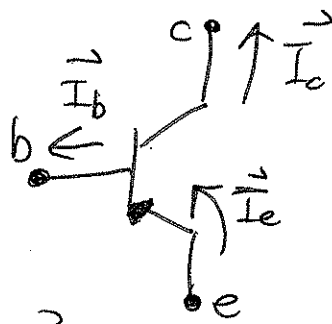

① Conservation of I

$$I_e = I_B + I_c$$

$$\text{let } \alpha = \frac{I_c}{I_e}$$


$$\text{or } I_e = \frac{I_c}{\alpha}$$

$$I_B = I_e \left(1 - \frac{I_c}{I_e} \right) = \frac{I_c}{\alpha} (1 - \alpha)$$

$$\frac{I_c}{I_B} = \frac{\alpha}{1 - \alpha} = \beta$$

Amount of current gain ...

Data :

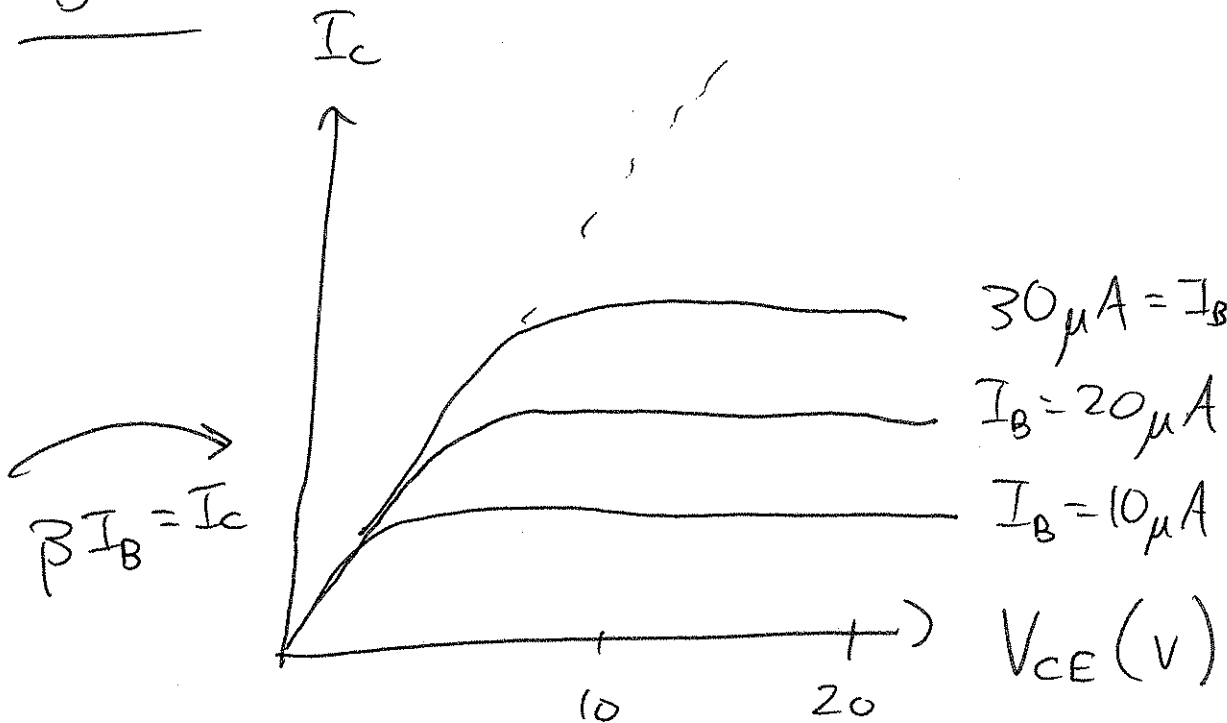

$$30 \mu A = I_B$$

$$I_B = 20 \mu A$$

$$I_B = 10 \mu A$$

$$V_{CE} (V)$$

↑ increase
 V_{base} ,
 I_B

(4)