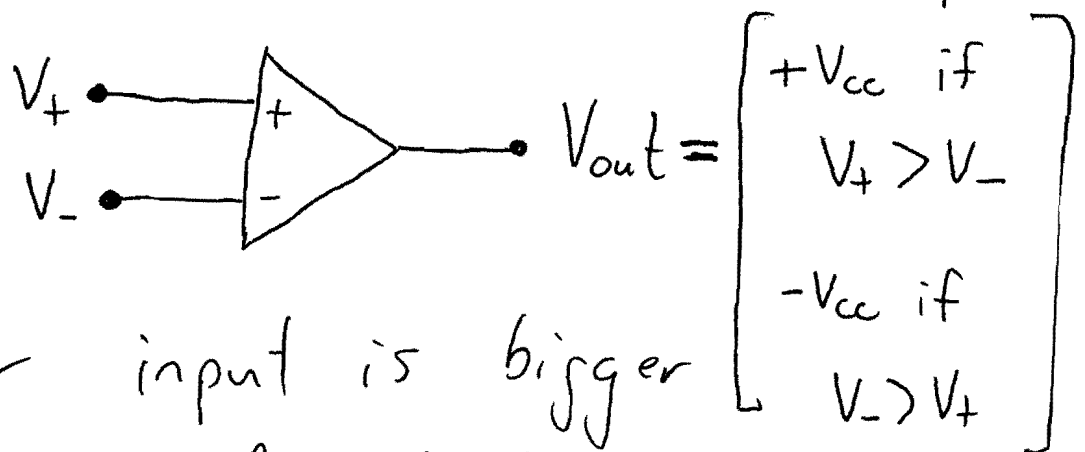



Comparator Circuits :

Think of a bare-bones op-amp setup,




Whichever input is bigger produces railed output in the same polarity because $V_{out} = G(V_+ - V_-)$ and $G \approx 10^5$.

Simple Comparator :

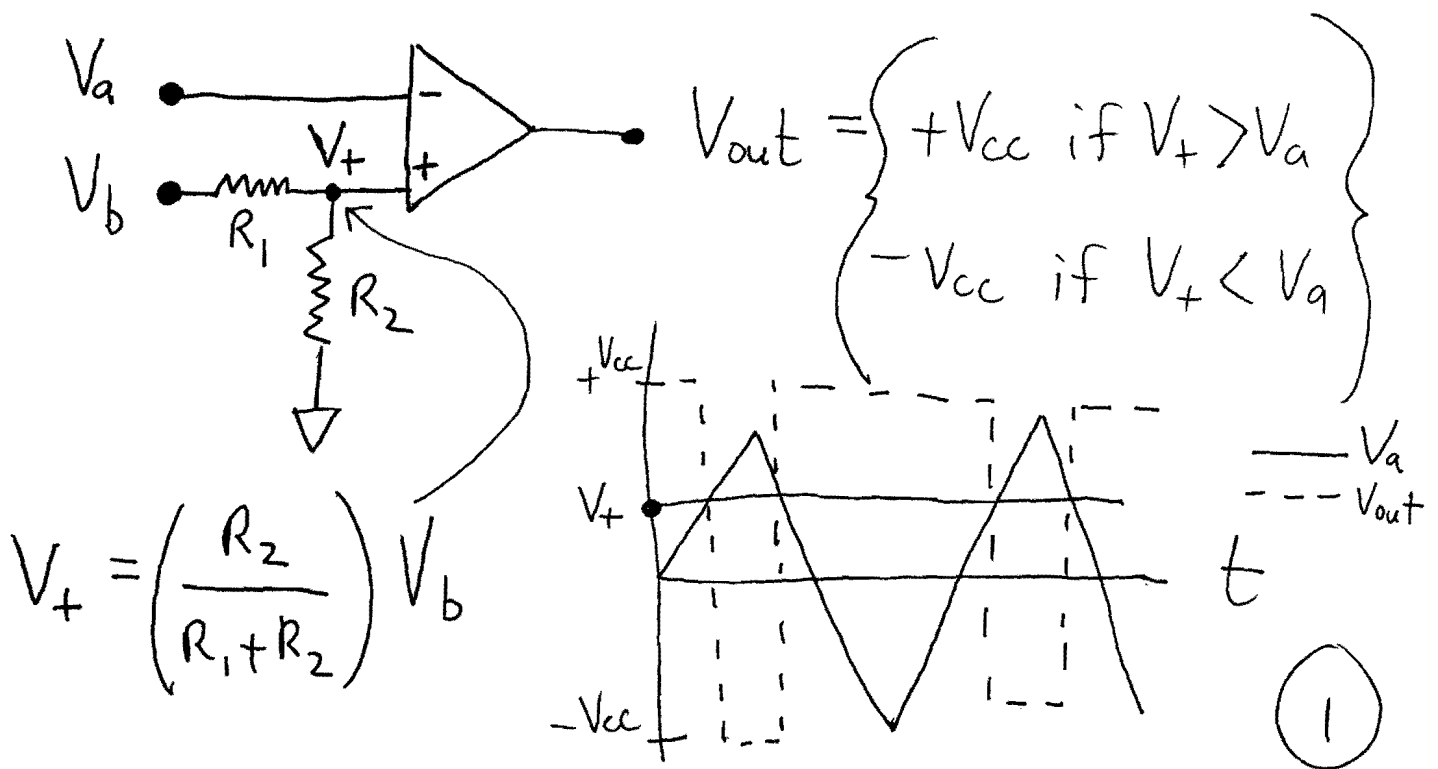

Schmitt Trigger Comparator :

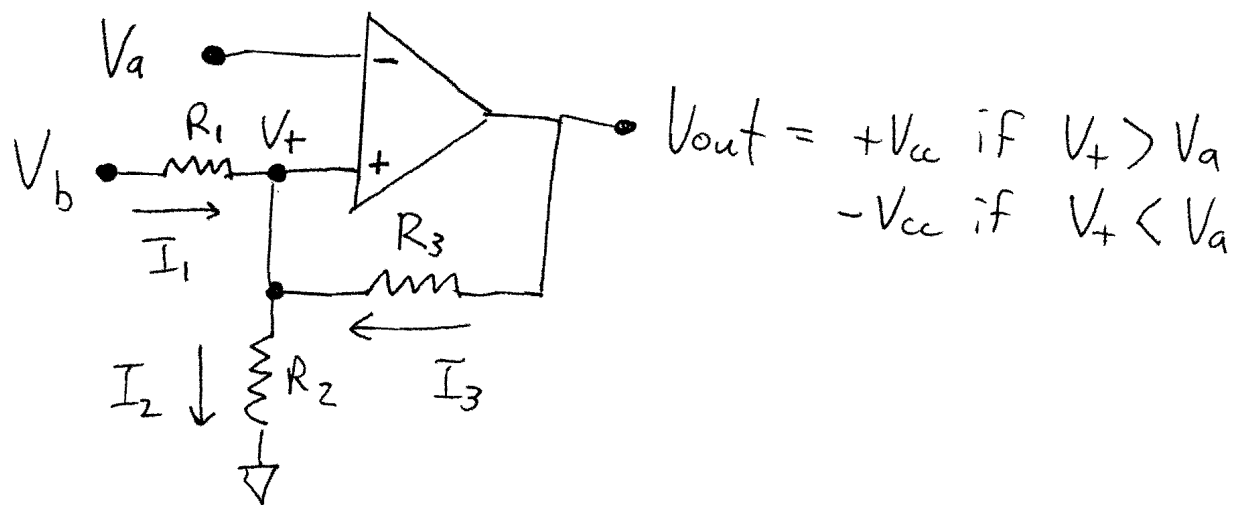

The Schmitt trigger is a comparator w/ positive feedback. V_+ can take on two different values depending on whether $V_{out} = \pm V_{cc}$.

Case 1 : ($V_{out} = +V_{cc}$)

$$\underbrace{I_1 + I_3}_{\text{Conservation of current}} = I_2$$

$$\frac{V_b - V_+}{R_1} + \frac{V_{cc} - V_+}{R_3} = \frac{V_+}{R_2}$$

(2)

which leads to :

$$\frac{V_b}{R_1} + \frac{V_{cc}}{R_3} = V_+ \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

when $V_{out} = +V_{cc}$

$$\left(R_{123} \right)^{-1}$$

$$V_+ = \frac{R_{123}}{R_1} V_b + \frac{R_{123}}{R_3} V_{cc}$$

Using the same conservation of current laws and $V_{out} = -V_{cc}$ yields: Case 2: ($V_{out} = -V_{cc}$)

$$V_+ = \frac{R_{123}}{R_1} V_b - \frac{R_{123}}{R_3} V_{cc}$$

when $V_{out} = -V_{cc}$