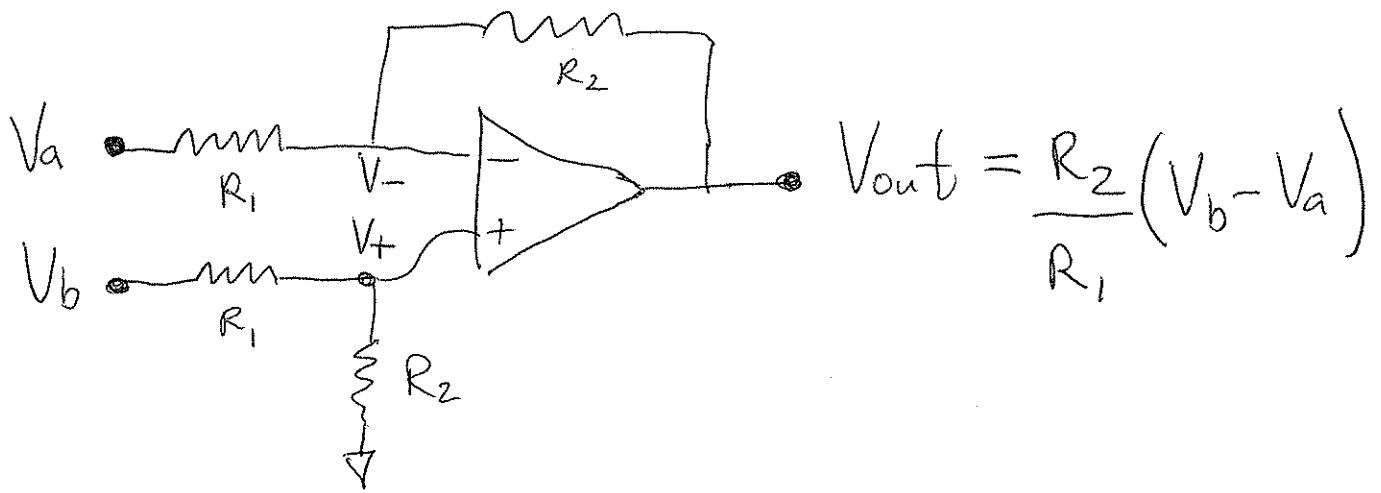


Difference Amplifier :



Calculate V_{out} using first principles.

Non-inverting input :

(Divider) $V_+ = \left(\frac{R_2}{R_1 + R_2} \right) V_b = f V_b \quad (1)$

Inverting input :

(\vec{I} conservation) $\frac{V_a - V_-}{R_1} = \frac{V_- - V_{out}}{R_2} \quad (2)$

(Solve for V_-)

$$V_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_a}{R_1} + \frac{V_{out}}{R_2}$$

$$V_- \left(\frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_a}{R_1} + \frac{V_{out}}{R_2} \quad (1)$$

$$V_-(R_1 + R_2) = R_2 V_a + R_1 V_{out}$$

$$V_- = \underbrace{\left(\frac{R_2}{R_1 + R_2}\right)}_{= f} V_a + \underbrace{\left(\frac{R_1}{R_1 + R_2}\right)}_{= f \frac{R_1}{R_2}} V_{out}$$

$$V_- = f V_a + f \frac{R_1}{R_2} V_{out} \quad (3)$$

Op-amp output :

$$V_{out} = G(V_+ - V_-) \quad \left. \begin{array}{l} V_+ = (1) \\ V_- = (3) \end{array} \right\}$$

$$V_{out} = G \left(f V_b - f V_a - f \frac{R_1}{R_2} V_{out} \right)$$

$$V_{out} = G f \left(V_b - V_a - \frac{R_1}{R_2} V_{out} \right)$$

$$V_{out} \left(1 + G f \frac{R_1}{R_2} \right) = G f (V_b - V_a)$$

Assuming $G f \frac{R_1}{R_2} \gg 1 \Rightarrow \left(1 + G f \frac{R_1}{R_2} \right) \approx G f \frac{R_1}{R_2}$

$$\boxed{V_{out} \approx \frac{R_2}{R_1} (V_b - V_a)} \quad (2)$$