

# Bipolar Junction Transistors and Applications

## Transistor Physics

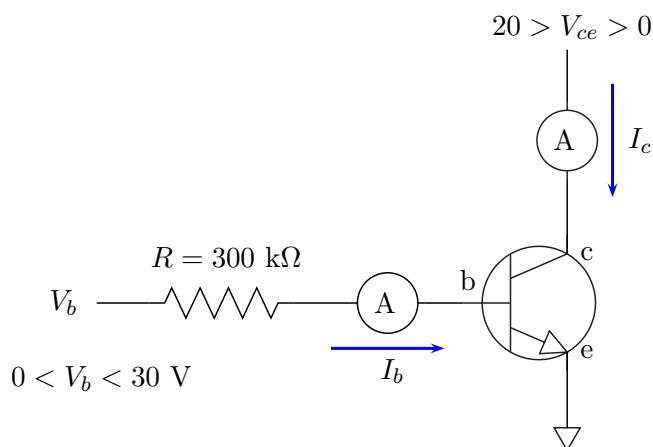


Figure 1: Measurement of  $\beta = I_c/I_b$  for an npn bipolar junction transistor.

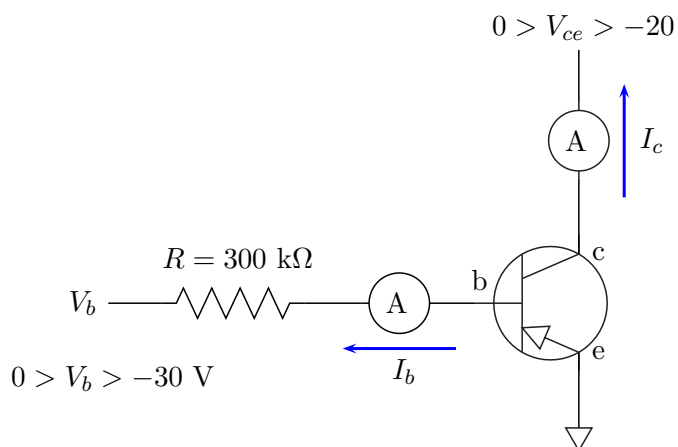


Figure 2: Measurement of  $\beta = I_c/I_b$  for a pnp bipolar junction transistor.

## Common Emitter Amplifier

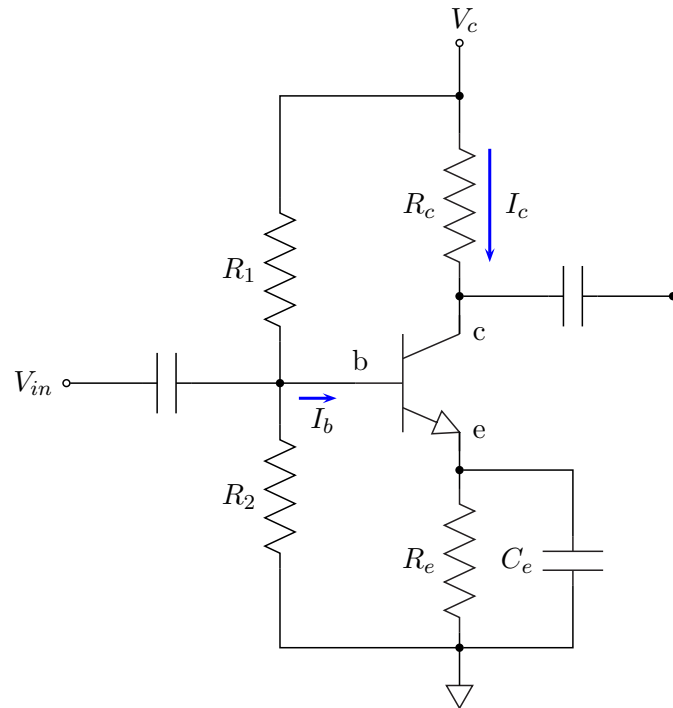


Figure 3: In the common emitter amplifier configuration the DC (zero frequency) operating point is determined by the DC bias current controlled by  $R_1$  and  $R_2$ .  $R_e$  provides the negative feedback necessary for thermal stability, and  $C_e$  provides an AC (finite frequency) path to ground. The high frequency gain is approximately  $-R_c/Z_{be}$ , where  $Z_{be}$  is the base-emitter impedance.

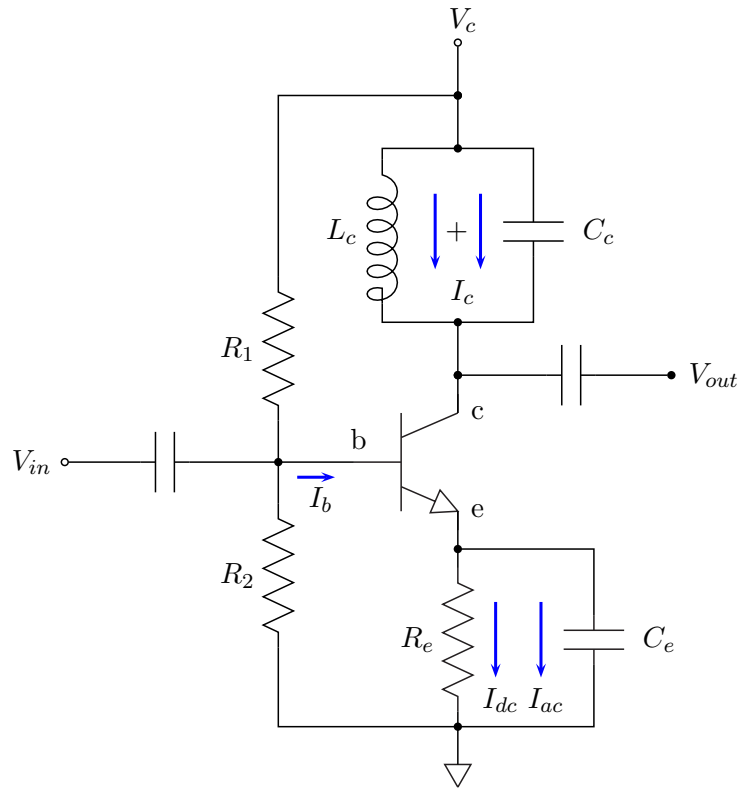


Figure 4: In the bandpass common emitter amplifier, the gain  $G(\omega) \simeq -Z_{L||C}/Z_{be}$  becomes large at the  $LC$  tank resonance frequency  $\omega_o = 1/\sqrt{LC}$  because  $Z_{L||C}(\omega_o)$  is very large.

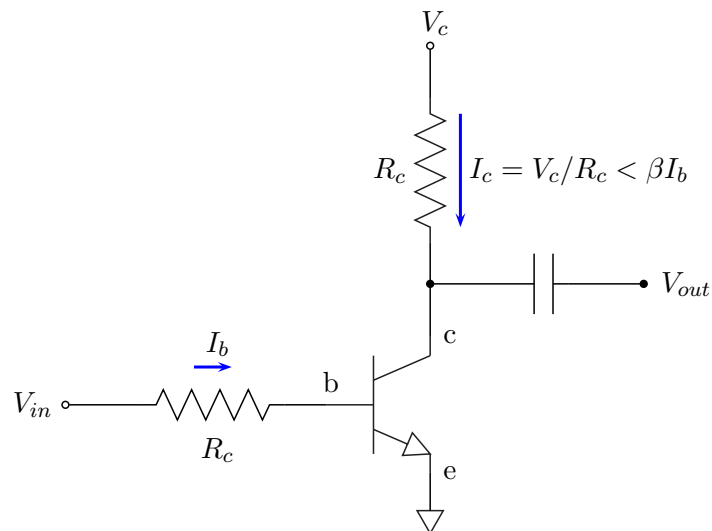


Figure 5: In the saturated common emitter amplifier configuration, known as the *saturated switch*, the base current is either zero or large enough so that the collector current is the maximum value of  $V_c/R_c$ .

## Common Collector Amplifier

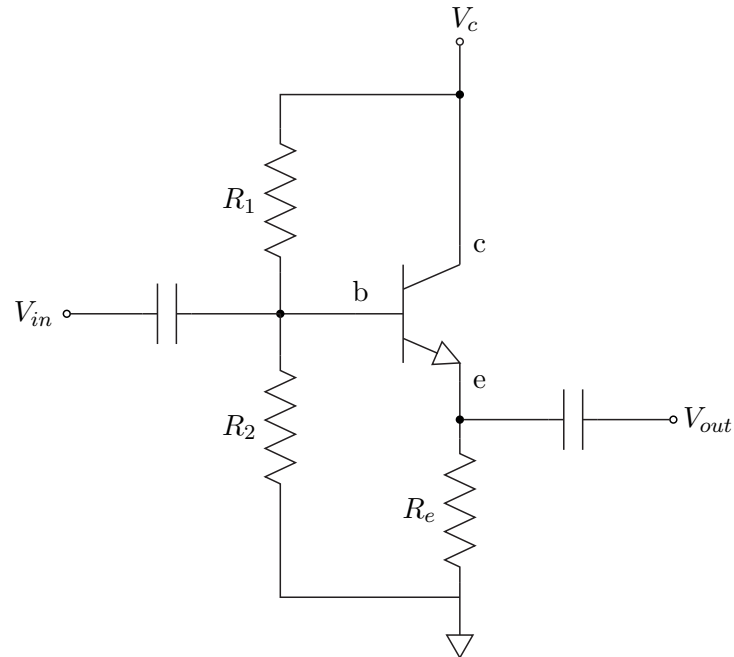


Figure 6: In the common collector amplifier configuration the negative feedback provided by  $R_e$  yields a gain of approximately 1, that is,  $V_{out} = V_{in} - 0.6 \text{ V}$ .

## Constant Current Source

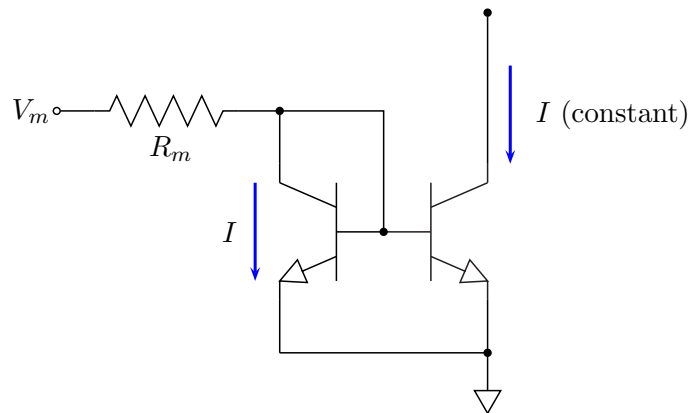


Figure 7: The *current mirror* provides a constant current for another circuit.  $I$  is determined by  $V_m/R_m$ .

## Differential Amplifier

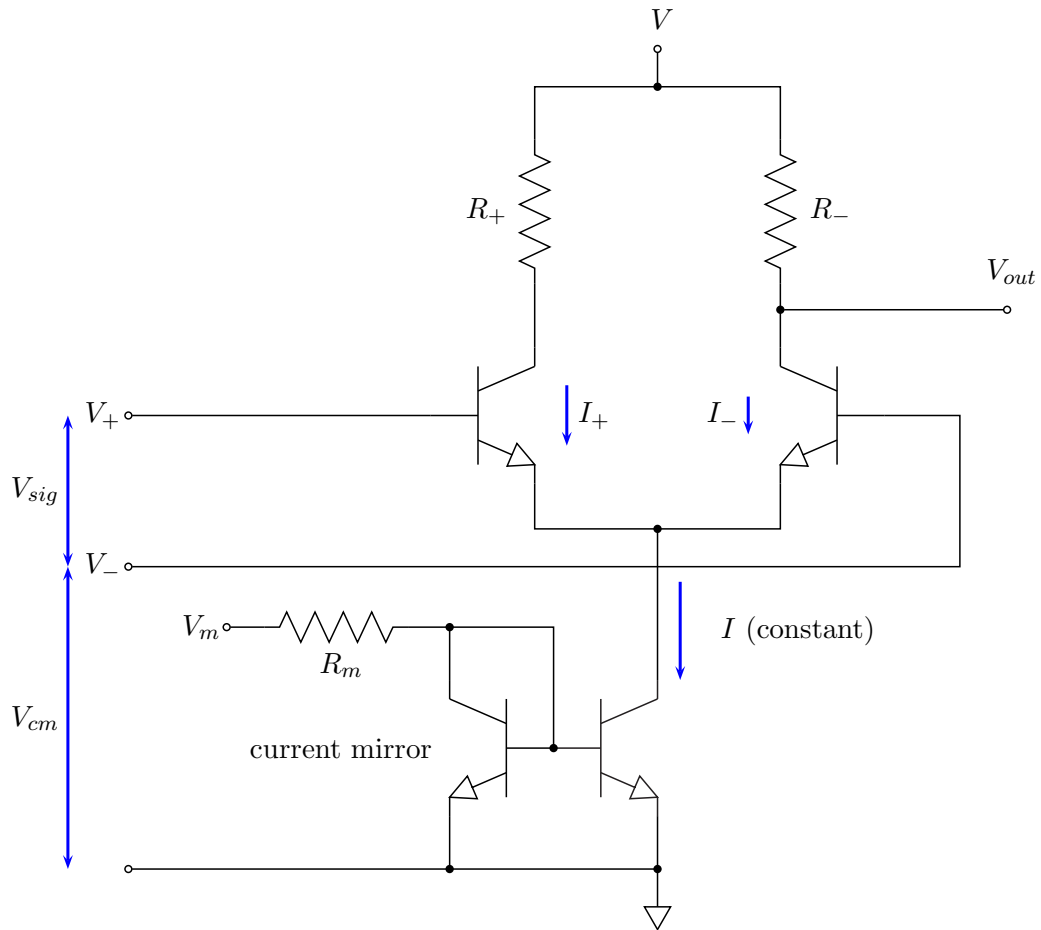


Figure 8: In the differential amplifier, the sum of the currents passing through the two transistors is held constant by the *current mirror*. The output signal is proportional to  $-(V_+ - V_-)$ , reminiscent of the operational amplifier. This circuit is used to provide gain while eliminating the *common mode* signal  $V_{cm}$ .

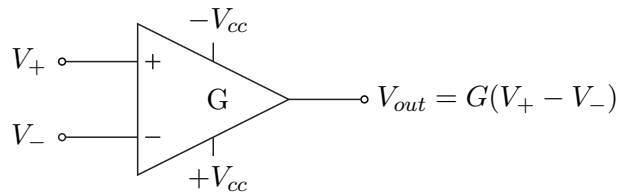


Figure 9: The *operational amplifier* is a differential amplifier with  $V_{out} = G(V_+ - V_-)$ .

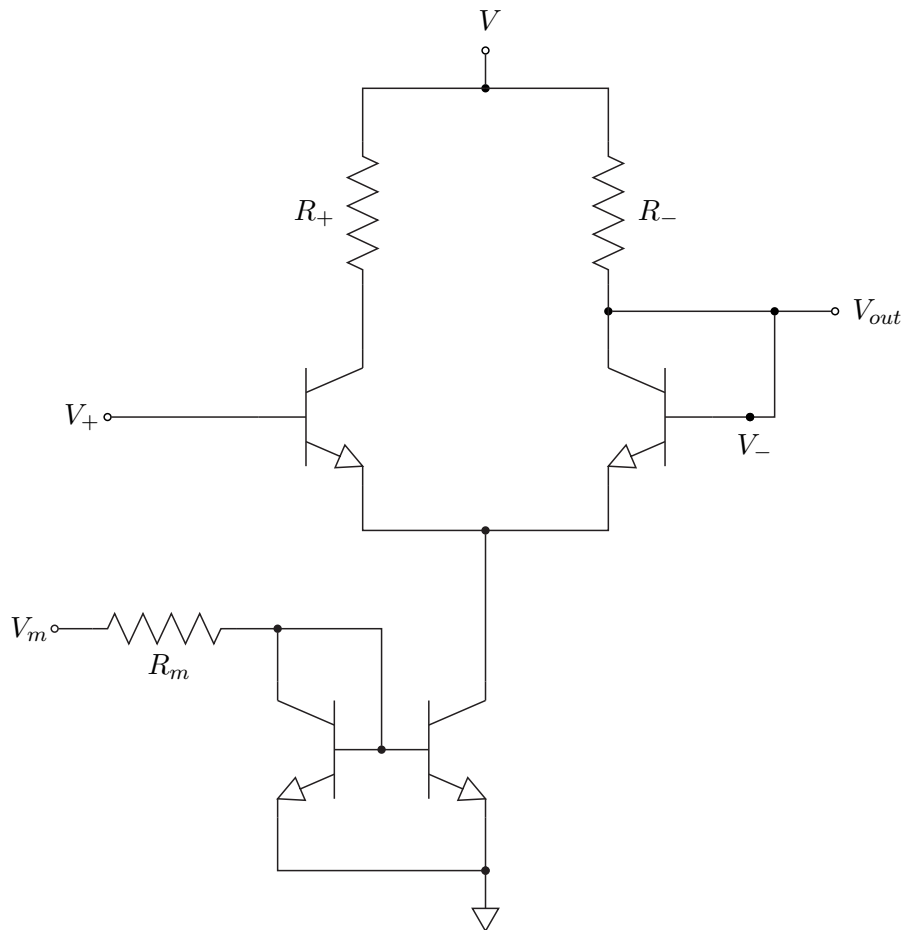


Figure 10: In the differential amplifier, the sum of the currents passing through the two transistors is held constant by the *current mirror*. The output signal is proportional to  $-(V_+ - V_-)$ , reminiscent of the operational amplifier. This circuit is used to provide gain while eliminating the *common mode* signal  $V_{cm}$ .

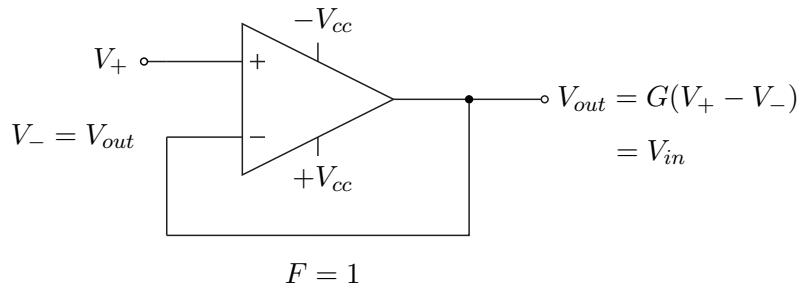


Figure 11: In the *noninverting unity gain configuration*, the output is fed back to the inverting input. The feedback fraction is  $F = 1$ , and the gain of the circuit is  $1/F = 1$ .

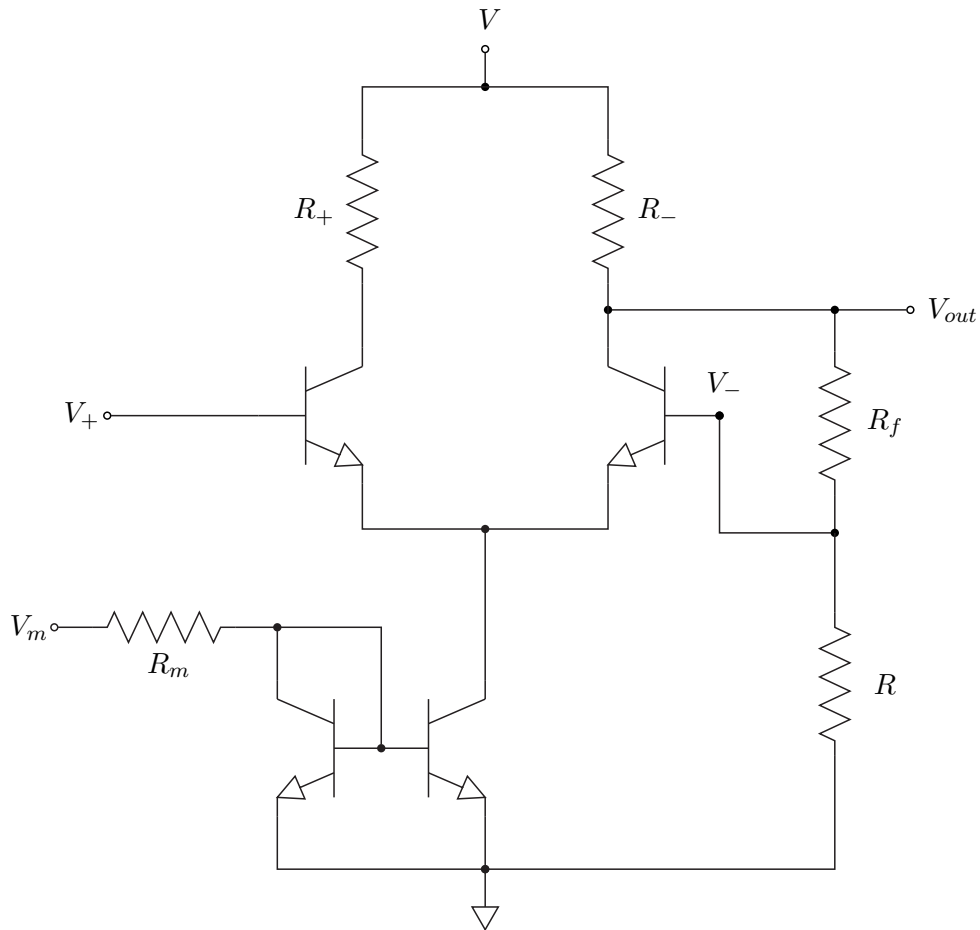


Figure 12: The use of negative feedback, where  $F$  is the feedback fraction, limits the gain of the differential amplifier to  $-1/F$  when  $|GF| \gg 1$ , where  $G$  is the open loop gain.

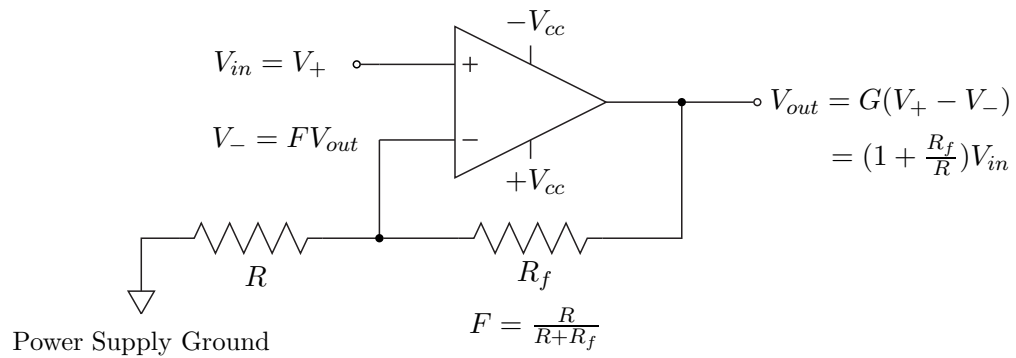


Figure 13: In the *noninverting operational amplifier configuration*, a fraction  $F$  of the output is fed back to the inverting input, and the gain of the circuit is  $1 + R_f/R$ .