


Fun with Flip-Flops :

Flip flops are the basic building blocks of memory systems, counters, serial to parallel conversion, digital data transmission, and arithmetic operations on binary numbers.

Basic Definition :

A flip-flop is a circuit with two output terminals and two stable output states.

NOR - truth table :

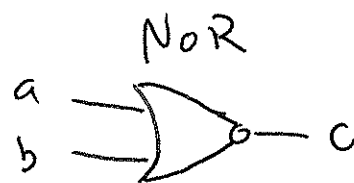


OR

a	b	c
0	0	0
1	0	1
0	1	1
1	1	1

NOR

a	b	c
0	0	1
1	0	0
0	1	0
1	1	0



RS - flip-flop w/ NOR gates

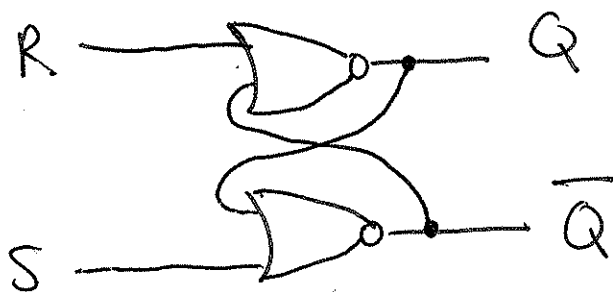


RS - flip flop truth table :

S	R	Q	\bar{Q}
0	0	1	0
0	0	0	1
1	0	1	0
0 0 0 0			
0	1	0	1
1	1	?	?
		0	0

Draw like this ↓

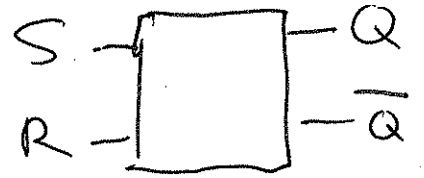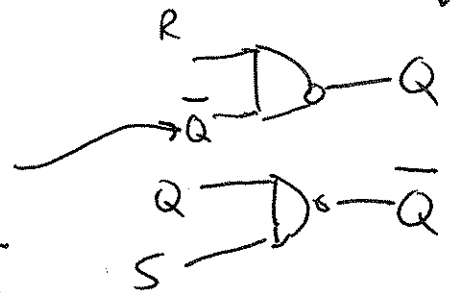

timing diagram :

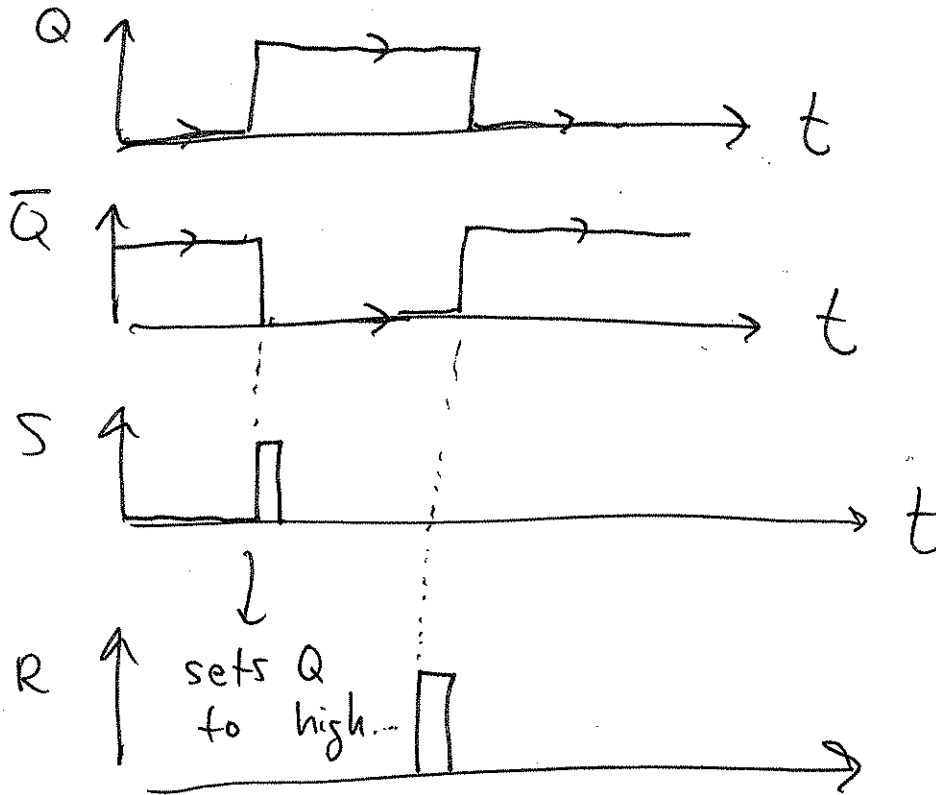

D-type Flip Flop :




"Data Latch" Flip-Flop has one data input and one clock.

(I) IF the clock is high, then Q is affected by D.

(II) IF clock = low, then Q is unaffected.

RS version :

circuit schematic :

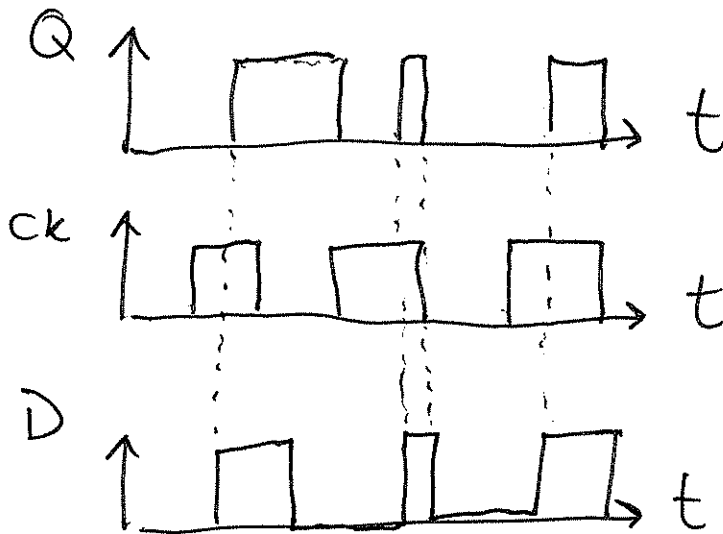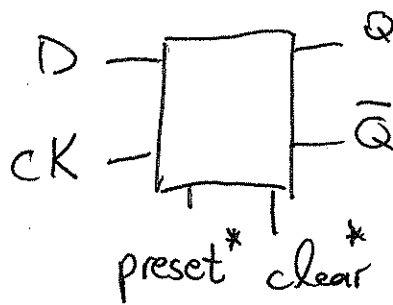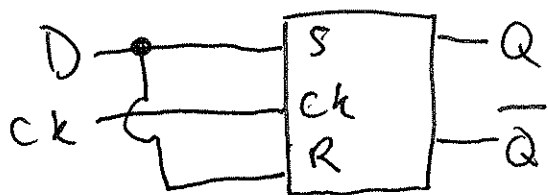


* active low

Lab Tasks:


- ① Verify the truth table.
- ② Build a "one shot" or "monostable multivibrator"

Draw timing diagrams:

ck, Q, \bar{Q} , CLR

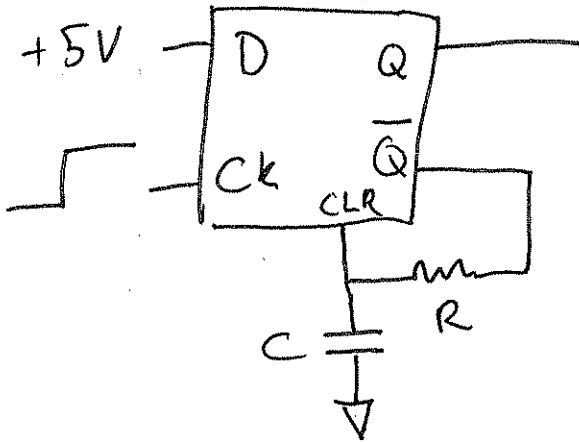


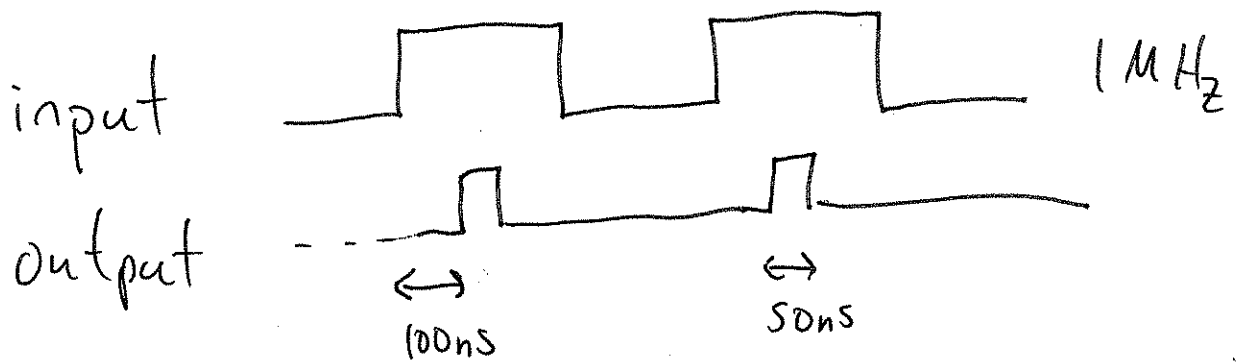- ③ Build a circuit that generates a 50ns pulse 100ns after an input pulse by using two one-shots.



- ④ Now try again using the 74LS123 chip.


⑤ Build the following shift register

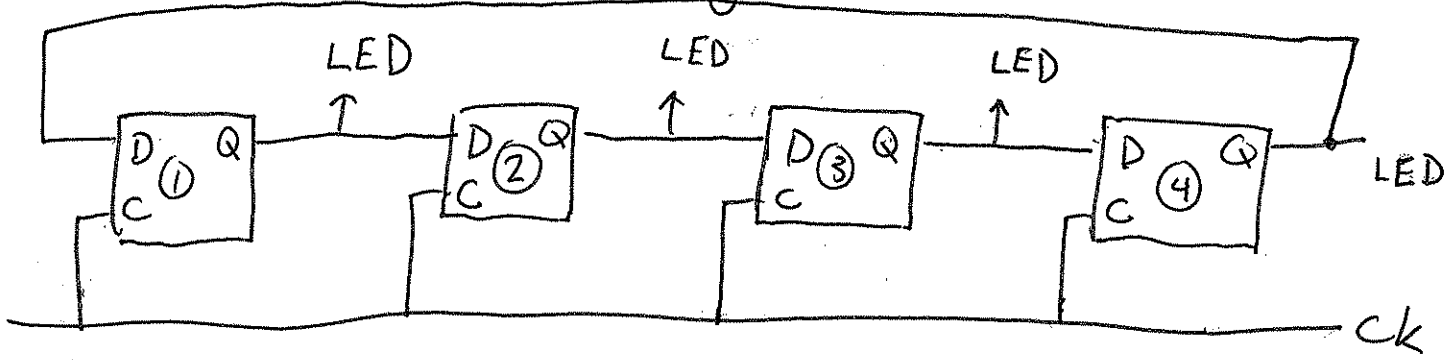

(a) with no clock set $Q_1 = 1, Q_2 = 1, Q_3 = 0, Q_4 = 0$.

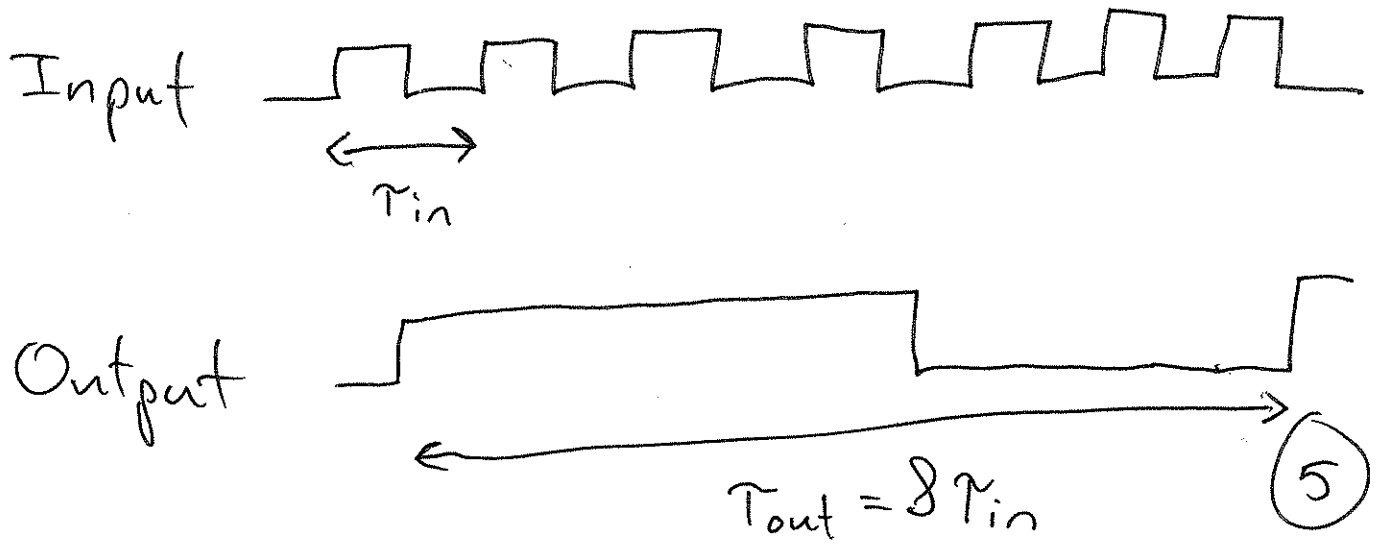(b) Apply a clock and observe and explain behavior.

⑥ Build a "divide by 2" circuit, why does this work? It's also a binary counter. (Add LED's to Q's to show this.)



⑦ Add a summing amplifier such that 3 bit counter is the digital input to a Digital to analog converter (DAC). Observe analog behavior and explain.